SUGGESTIONS AND PROCEDURE FOR MAKING A SECTIONALIZING STUDY

by
Bruce O. Watkins
Engineer, Technical Standards Division

Assisted by
Donnan E. Basler
Assistant Engineer, Technical Standards Division
James R. Oberholtzer
Associate Engineer, Technical Standards Division

U. S. DEPARTMENT OF AGRICULTURE
RURAL ELECTRIFICATION ADMINISTRATION
TECHNICAL STANDARDS DIVISION

Technical Standards Bulletin #4
August 1, 1941

SUMMARY

This bulletin outlines a procedure for making sectionalizing studies on REA systems, and contains suggestions for selecting sectionalizing equipment.

All analyses not specifically pertinent to rural circuits have been eliminated, resulting in complete and definite instructions for a sectionalizing study on a rural system of the REA type. The bulletin is written partly in the form of a textbook and partly in the form of instructions on method and procedure. Every effort has been made to make the text as simple as possible; knowledge of symmetrical components, or even of vector algebra, is unnecessary. A sample problem is given as an aid in understanding the text, which the reader is urged to follow before attempting to apply it to an actual case.

The engineer familiar with symmetrical components will find that some of the formulas in this text have a different form than the familiar ones. These changes have been made in the interest of simplicity for the special case of REA systems. For the purpose of simplification, various limitations were established. These simplifications and limitations are explained in the text, and should be noted carefully by anyone solving an actual problem.

The bulletin is divided into various parts as follows:

SUGGESTIONS AND PROCEDURE FOR MAKING A SECTIONALIZING STUDY

It is advisable to read this entire paper and to go through the example before attempting an actual study. In order to provide ease in checking, engineers making sectionalizing recommendations to REA projects should submit the study in the same general form as shown herein, using listed impedance values, unless local conditions, or other factors indicate that such is not advisable. In these cases, the engineer should submit the basis for his study, and the reasons for such differences.

Sectionalizing studies are not difficult, and all formulae have been reduced to simple forms.

I. Data Necessary

In order to make a complete sectionalizing study of a project, definite data on various items must be obtained from the project. These items are outlined in form TS-5, pages 26 - 29 (Formerly Form EO-19R). All of these data should be available before attempting a study, as lack of any will delay the work.

For a small REA or municipal plant, the following data should be obtained from the machinery manufacturer:

Unit No.	Kva Capacity	% Direct Axis Reactance Transient	% Direct Axis Reactance Synchronous	% Negative Sequence Reactance
1				
2				
3				
4				
5				

It is also necessary to obtain time-current characteristics for all sectionalizing devices used on the project. These are explained more in detail later.

II. Location of Sectionalizing Devices

The first step is to make a tentative location of sectionalizing devices. Individual judgment must be used for each case, but the following points may be helpful:

1. If two or more main feeder lines go out from the substation, a sectionalizing device should be placed on each line. In other words, trouble on one line should not affect other main lines. In many cases, a set of cut-outs, or breakers for each line, will be preferable to only one set of cut-outs or breakers for the entire substation. In some cases, a quarter or half mile of double circuit line with one circuit overbuild will allow a division of feeders at the substation, with consequent operating advantages.

2. Branch lines over 4 or 5 miles in length should have sectionalizing devices. (Exceptions: where reclosing breakers or fuses are used.)

3. Where main lines branch, a sectionalizing device should be used in each line at the junction point.

4. The device should be accessible from highways open the year around.

5. The device should protect important loads (be beyond the transformer feeding the load).

6. Any branch line exposed to hazardous conditions (trees, etc.) should be separated from the remainder of the system by a reclosing device, if possible.

7. The device should be located near a member with a phone, if possible.

III. Short Circuit Currents

The next step is to calculate the approximate short-circuit currents on the system. Important - this discussion will assume a 60-cycle system with multigrounded neutral conductor with substation transformers connected delta on the supply side and wye on the load side. The REA system is also considered radial (i.e., no connected loops). For any other conditions, write REA, giving details.

Two types of fault currents should be computed, the maximum fault current and the minimum fault current. The former assumes all generating machines are connected, and zero fault resistance. The latter assumes the minimum number of generators, and some fault resistance. These should be computed for each sectionalizing point, including the substation, and at the ends of the longest sections.

It is generally possible, after some practice, to estimate fault currents for intermediate points with sufficient accuracy after a number of representative faults have been calculated.

Fuses are usually coordinated using the maximum fault currents. Minimum currents are used to make certain that sectionalizing devices will operate satisfactorily under all conditions. In particular, the substation transformers must be protected against all fault currents on the system. Although the general method of calculation is the same for both maximum and minimum fault values, the immediate discussion will concern the maximum values.

There are four possible types of faults, three-phase, double line-to-ground, line-to-line, and single line-to-ground. The first three can occur only on three-phase or "V" circuits, and even on these circuits usually only single line-to-ground faults will occur, due to the multigrounded construction.

This discussion will cover methods of calculation for line-to-ground, three-phase and line-to-line faults. For double line-to-ground faults, reference is made to "Symmetrical Components", by Wagner & Evans, McGraw Hill.

5. Where main line branch, a sectionalizing device should be used in each line at the junction point.

4. The device should be accessible from sidewalks upon the near ground.

3. The device should protect important loads (be beyond the transformer feeding the load).

6. Any branch line crossed to hazardous conditions (trees, etc.) should be separated from the remainder of the system by a reclosing device, if possible.

7. The device should be located near a member with a phone, if possible.

III. Short Circuit Currents

The next step is to calculate the appropriate short-circuit currents on the system. Important - this discussion will assume a distribution system with multigrounded neutral conductor with substation transformers connected delta on the supply side and wye on the load side. The FEA system is also considered radial (i.e., no connected loops). For any other conditions, write FEA, giving details.

Two types of fault currents should be computed, the maximum fault current and the minimum fault current. The former assumes all generating machines are connected, and zero fault resistance. The latter assumes the minimum number of generators, and zero fault resistance. These should be computed for each sectionalizing point, including the substation, and at the ends of the longest sections.

It is generally possible, after some practice, to estimate fault currents for intermediate points with sufficient accuracy after a number of representative faults have been calculated.

Fuses are usually coordinated using the maximum fault currents. Minimum currents are used to make certain that sectionalizing devices will operate satisfactorily under all conditions. In particular, the substation transformers must be provided adequate all fault currents on the system. Although the general method of calculation is the same for both maximum and minimum fault values, the immediate discussion will concern the maximum values.

There are four possible types of faults, three-phase, double line-to-ground, line-to-line, and single line-to-ground. The first three can occur only on three-phase or "Y" circuits, and even on these circuits usually only single line-to-ground faults will occur, due to the multigrounded neutral.

This discussion will cover methods of calculation for line-to-ground, three-phase and line-to-line faults. For double line-to-ground faults, reference is made to "Symmetrical Components", by Wagner & Evans, McGraw Hill.

The following set of symbols is used:

$I_{s(L-L)}$ = Line-to-line fault current in amperes on supply side at the substation.
$E_{s(L-L)}$ = Line-to-line voltage in volts on supply side of substation.
I_{3s} = Three-phase fault current in amperes on supply side at the substation.
I_L = Fault current on load side (REA side).
E_L = Line-to-ground voltage on load side of substation.
R_s = Equivalent resistance per phase of source at load (REA) voltage.
X_s = Equivalent reactance per phase of source at load voltage.
R_t = Resistance per phase of substation transformers at load voltage.
X_t = Reactance per phase of substation transformers.
Z_t = Impedance per phase of substation transformers.
R_L = Resistance per phase of REA distribution line (multigrounded).
X_L = Reactance per phase of REA distribution line (multigrounded).
Z = Total impedance per phase of distribution line, source and substation.
X_1, X_2, X_3 = Reactances of individual machines at load voltage (either direct-axis transient or negative sequence).
X_m = Resultant reactance of all machines running in parallel.
n = Number of machines.
KVA_1 = KVA capacity of individual machine (total).
KVA_t = Total KVA capacity of all machines.

There are three main components of the impedance to the fault: (A) the impedance of the source; (B) the impedance of the substation, and (C) the impedance of the REA distribution lines.

A. Line-to-Ground Faults

1. <u>Source Impedance</u>

(a) Large system

$$X_s = \frac{(E_{s(L-L)})}{(I_{s(L-L)})} \quad \frac{(E_L)^2}{(E_{s(L-L)})^2} \quad \text{or } X_s = \frac{(E_L)^2}{I_{s(L-L)}E_{s(L-L)}} \text{ ohms.} \qquad (1)$$

assume $R_s = 0$, or take an appropriate ratio between R and X based on judgment.

If only the three-phase fault current is given,

$$X_s = \left(\frac{2}{\sqrt{3}}\right)\left(\frac{(E_L)^2}{I_{3s}E_{s(L-L)}}\right) \qquad (1a)$$

assume $R_s = 0$, (See note under (1) above)

(Formula (1) is the more accurate)

The following set of symbols is used:

$I_s(L-L)$ = Line-to-line fault current in amperes on supply side of the substation.

$E_s(L-L)$ = Line-to-line voltage in volts on supply side of substation.

I_{3s} = Three phase fault current in amperes on supply side of the substation.

I_L = Fault current on load side (REA side).

E_L = Line-to-neutral voltage on load side of substation.

R_s = Equivalent resistance per phase of source at load (REA) voltage.

X_s = Equivalent reactance per phase of source at load voltage.

R_t = Resistance per phase of substation transformers at load voltage.

X_t = Reactance per phase of substation transformers.

R_L = Resistance per phase of REA distribution line (multigrounded).

X_L = Reactance per phase of REA distribution line (multigrounded).

Z = Total impedance per phase of distribution line, source and substation.

X_1, X_2, X_3 = Reactances of individual machines at load voltage (either transient or negative sequence).

X = Equivalent reactance of all machines running in parallel.

n = Number of machines.

KVA_i = KVA rating of individual machine (total).

KVA_t = Total KVA rating of all machines.

There are three main components of the impedance to the fault: (A) the impedance of the source; (B) the impedance of the substation, and (C) the impedance of the REA distribution line.

A. Line-to-Ground Fault

1. Special Impedance

(a) Large system

$$X_s = \frac{E_s(L-L)}{I_s(L-L)} \quad \frac{E_s(L-L)}{I_{3s}} \quad \text{or} \quad X_s = \frac{E_s(L-L)}{I_s(L-L)} \quad \text{ohms.} \qquad (1)$$

Assume $R_s = 0$, or take an appropriate ratio between X_s and R based on system.

Then the three-phase fault current is given:

$$I_{3s} = \left(\frac{E_s(L-L)}{X_s}\right) \qquad (2)$$

Assume $R_s = 0$. (See note under ...)

(Formula (1) is the more accurate ...)

(b) Small system or REA plant

$$X_1 \text{ (ohms)} = \frac{X_1(\text{Percent})(E_L)^2(3)}{KVA_1\ (100{,}000)} \qquad (2)$$

(Use X_1 = direct-axis transient reactance for maximum fault current)

X_2 and X_3 can be found in a similar manner.

$$\text{Then, } \frac{1}{X_m} = \frac{1}{X_1} + \frac{1}{X_2} + \frac{1}{X_3} + - - - - \qquad (3)$$

If all machines are alike, $X_m = \frac{X_1}{n}$. (n should be maximum for maximum fault current) (3a)

Next determine the <u>negative sequence reactances</u> by using formulas (2) and (3) above, only with the percent negative sequence values.

$$\text{Then } X_s = \frac{(X_m\ (\text{transient}) + X_m\ (\text{neg. seq.}))}{3} \qquad (4)$$

X_m values must be in ohms.

If machine reactances are not obtainable, the following values may be used for approximation. (To be used only with discretion.)

Slow speed Diesel - driven or reciprocating steam engine driven generators:

(1) Direct-axis transient reactance = 35%
(2) Negative sequence reactance = 22%
(3) Synchronous = 110%

Non - salient pole turbine - driven generators
(1) Direct-axis transient reactance = 2 pole 15% 4 pole 23%
(2) Negative sequence reactance = 2 pole, 11% 4 pole 16%
(3) Synchronous reactance = 110%
Machine resistance can be neglected

If the plant is some distance from the REA substation, the resistance and reactance of the tie line must be obtained. This can be done by using handbook values (see Standard Handbook for Electrical Engineers, McGraw Hill, for example). for the resistance and reactance of the line, using the conductor sizes and spacings of the line. Simply multiply <u>twice</u> the line distance in miles by the resistance and by the reactance (positive sequence) of the line per phase per mile. Convert each of these values separately to REA voltage by multiplying each by $\frac{E_L^2}{(E_{s(L-L)})^2}$.

The above assumes a constant voltage along the tie line. If there is another voltage transformation in this tie line, the resistance and reactance of <u>each section</u> should be computed as above,

using the voltage for each section and the resistance and reactance of the extra transformer added, as shown below.

The total X_s equals X_s from (4) plus the reactance determined above and R_s equals the resistance as determined above.

2. Substation Transformer Impedance

$$Z_t \text{ (ohms)} = \frac{Z_t \text{ (percent) } (E_L)^2}{\text{(kva per phase) } (100{,}000)} \qquad (5)$$

$$X_t = 0.97\ Z_t$$

$$R_t = 0.25\ Z_t$$

If Z_t is not known, approximate Z_t = 5% for transformers 100 Kva or over
Z_t = 4% for transformers less than 100 Kva

3. REA Line Impedance

To find the line-to-ground impedance to any point on the system, use the following values of impedance per mile:

Copper Conductivity Size	R_L	X_L
1/0	0.723	1.124 per mile
2	1.00	1.22 " "
4	1.63	1.31 " "
6	2.45	1.46 " "
8	3.74	1.55 " "
9½	5.04	1.67 " "
11	7.36	1.704 " "

Multiply each of the above values by the number of miles of each conductivity size from the substation to the point being considered.

(A table is given which will facilitate this. See table I for Average REA Single Phase Line Impedance, page 35)

Note: The above impedance values are for multigrounded lines and are average values. If more accuracy is desired, use the appropriate values in the single phase impedance column of table II titled "Impedance of REA Lines - Standard REA Spacings," page 36.

If two or more different sized conductors are used from the substation to the point, add the total resistance to the first size to the resistance of the next size to the point, and add the total reactance of the first size to the reactance of the next size, etc.

4. Total of Impedances

To find the total impedance to each point, add the reactance of the source as determined under (1), to the reactance of the substation transformer 2, plus the reactance of the REA line 3. Add the resistance of the source 1 to the resistance of the substation 2, plus the resistance

of the REA line to the point 3. Then, total impedance to the point equals the square root of the sum of the square of the total resistance plus the square of the total reactance.

$$Z = \sqrt{R^2 + X^2} \tag{6}$$

$$\text{and } I_L = \frac{E_L}{Z} \tag{7}$$

Ordinarily any drop in E_L is neglected, and E_L is taken as the voltage at the substation. The circle diagram charts in the text may be used instead of formulas (6) and (7) (pages 37 and 38.)

B. Three Phase Faults

1. Source Impedance

(a) Large System

$$X_s = \frac{E_{s(L-L)}}{(I_{3s})\ (\sqrt{3})} \frac{(E_L)^2\ (3)}{E_{s(L-L)}^2}$$

$$\text{or } X_s = \frac{(E_L)^2\ (\sqrt{3})}{(I_{3s})\ (E_{s(L-L)})} \tag{8}$$

Where I_{3s} is the three-phase fault current at the substation.

(b) Small system or REA plant use direct axis transient reactance only, and apply formula (2).

Note: For any tie line, use three times the positive sequence values only, and convert to REA voltage by multiplying by

$$\frac{E_L^2}{E_{s(L-L)}^2}.$$

2. Substation Impedance

Use formula (5) as before.

3. REA Line Impedance

Use resistance and reactance values under impedance to positive or negative sequence current for three-phase lines in table II entitled "Impedance of REA Lines", page 36.

With these values, proceed as before using formulas (6) and (7).

C. Line-to-Line Faults

1. Source Impedance

(a) Large System

$$X_s = \frac{E_L^2 \sqrt{3}}{I_{(L-L)}\ E_{s(L-L)}} \tag{9}$$

(b) Small system or REA plant.

For X_1 and X_2 use formula (2)

$$X_s = \frac{X_1 \text{ (transient)} + X_2 \text{ (negative sequence)}}{\sqrt{3}} \tag{10}$$

Note: For any tie line, use $2\sqrt{3}$ times the positive sequence line values, and convert to REA voltage by multiplying by $\frac{E_L^2}{E_{s(L-L)}^2}$

2. Substation

$$Z_t \text{ (ohms)} = \frac{Z_t \text{ (percent) } (E_L)^2(2)}{(\text{KVA per phase})(100{,}000)\sqrt{3}} \tag{11}$$

3. Lines

Multiply impedance to positive or negative sequence currents,

Table II, by $\frac{2}{\sqrt{3}}$ (12)

Then $Z = \sqrt{R^2 + X^2}$

and $I_L = \frac{E_L}{Z}$ as in formulas (6) & (7)

D. Fault current on Supply Side

A current on the load side of the substation of course causes a current to flow on the supply side. The following formulas apply for delta-wye banks only.

1. For line-to-ground fault

$$I_s = \frac{E_L}{E_{s(L-L)}} I_L \quad * \tag{13}$$

2. For three phase fault

$$I_s = \frac{E_L\sqrt{3}}{E_{s(L-L)}} I_L \tag{14}$$

3. For a line-to-line fault

$$I_s = \frac{2\,E_L}{E_{s(L-L)}} I_L \tag{15}$$

* Note: (I_s is not necessarily the same in all three phases. The formulas give the maximum supply currents in any one phase)

Ordinarily, it is only necessary to calculate the three phase and line-to-line fault currents at the end of the section controlled by the sectionalizing devices at the substation.

Minimum Values

In computing minimum fault values, simply use the minimum number of machines under 1, source impedance. In addition, if the capacity of the plant is about the same as the demand on the project (i.e., the plant serves little or no other load besides the project), the positive sequence reactance used in formula (2) should be increased to allow for machine decrement. A value between the transient and the synchronous may be used, the exact figure depending on judgment. In most cases of this kind, REA has used a value of 50 to 55% for conservative results. For large sources of supply, the supply impedance is small and the decrement is therefore relatively unimportant. Also, add a value for effective fault resistance to the R component. This value is subject to judgment and may be from 0 to 1000 ohms, but 30 or 40 ohms resistance are average values to use for line-to-ground faults. 40 ohms is a more conservative value, and is recommended. For other types of faults, neglect fault resistance.

Such factors as decrement, automatic voltage regulators, load, etc., have been neglected or assumed in the above outline, since too much labor is required to accurately evaluate these effects. For ordinary work, the slide rule is sufficiently accurate for all practical purposes.

The engineer should take care in using special slide rules or nomographs in calculating fault currents on REA projects, since most of these devices are not calibrated for calculations on multigrounded circuits.

Furthermore, such devices are based on the assumption that the impedances may be added algebraically, which results in a rather large error on wire sizes used on REA projects.

Typical decrement curves in handbooks should also be used with caution, as these neglect circuit resistance and assume no automatic voltage regulation.

After calculation of the short circuit currents, put the values directly on the map opposite each sectionalizing or other point. (See Example).

IV. Selection of Sectionalizing Devices

Automatic and non-automatic devices can be used. Under automatic, the two general groups are (1) fused cut-outs and (2) reclosing breakers. Non-automatic devices can be used in many cases where automatic operation is not possible, and consist of disconnect switches of all descriptions.

The fused cut-out may be single-, two-, or three-shot. In any case, the fuse link or links must be replaced after blowing. The reclosing breaker, on the other hand, will operate indefinitely without attention, unless a permanent fault, such as a conductor break occurs.

Of the automatic devices, fused cut-outs will generally be cheaper in first cost, but will be more expensive to maintain than breakers. Single-shot

[illegible], it is only necessary to calculate the three phase [illegible] [illegible] at the end of the section [illegible] by the [illegible] of the [illegible].

[illegible]

[illegible] the [illegible] use the minimum [illegible] [illegible] in formula (2) [illegible] between [illegible] the [illegible] has used [illegible] of supply, the supply [illegible] small [illegible] relatively [illegible] effective [illegible] judgment [illegible] for [illegible] conservative value, [illegible] recommended [illegible] of results, [illegible]

Such factors as [illegible], automatic voltage regulators, load, etc., have been neglected or [illegible] in the above outline, since too much labor is required to compute [illegible] these effects. For ordinary work, the slide rule is sufficiently accurate for all practical purposes.

The engineer [illegible] take [illegible] in using special slide rules or nomographs in calculating fault currents on REA projects, since most of these devices are not calibrated for calculation on multigrounded circuits.

Furthermore, such devices are based on the assumption that the impedances may be added algebraically, which results in a rather large error on wire sizes used on REA projects.

Typical decrement curves in handbooks should also be used with caution, as these neglect circuit resistance and assume no automatic voltage regulation.

After [illegible] of the fault currents, put the values directly [illegible] opposite each [illegible] that point. (See Example).

[illegible] of Se[illegible]

Automatic [illegible] automatic. The [illegible] general [illegible] (1) automatic and (2) [illegible] breakers. The [illegible] in many [illegible] switches [illegible]

The fused cutouts [illegible] two, or three-shot. In the case, the fuse links must be replaced [illegible] The reclosing breakers, [illegible] to the [illegible] with [illegible] permanent [illegible]

If the [illegible] will necessarily be [illegible] first [illegible] will be [illegible] operators. [illegible]

cut-outs can be coordinated more easily than two or three-shot cut-outs, but on the other hand cause more outage time. Only a complete study of all factors can determine the best combination. Generally, at least two-shot cut-outs should be placed on every important branch line. In cases where gapped transformers are used, reclosing breakers must be used to sectionalize the branch with these transformers and protect the remainder of the system against outages on lightning flashover. In other cases, it may be the judgment of the engineer that reclosing breakers will pay for themselves in reduced maintenance costs. Since temporary faults are usually very much in the majority, single-shot cut-outs will cause a great many unnecessary outages. All other things being equal, it is preferable to spend available funds on reclosing devices of some kind, even if fewer devices are installed.

Switches or disconnecting cut-outs save a great deal of outage time by allowing the linemen to isolate the faulty section and restore service to the remainder of the system.

V. Selection of Fuse Sizes

For coordination purposes, it is absolutely essential that only one make of fuse link be used throughout in the lines on the load side of the substation. The fuse on the supply side may, and generally will, be different.

The first step is to obtain curves and tables of the fuse links to be used on the lines. The curves necessary are (A) the total clearing time curves and (B) the "damaging" time curves. Curves (B) may not be necessary if the table mentioned below (pages 57 & 58) is obtained. These curves show current plotted against time for various size fuses.

(A) Total clearing time curves: These curves are available from most fuse manufacturers. If not available, the manufacturer will generally give a melting time curve and an "arcing" time curve or table. The total clearing time curves can be prepared by adding the arcing time to the melting time for each short circuit current, and for each fuse size. These curves represent, for each fuse size, the total time taken for the fuse to clear the circuit for various fault currents. (See page 60.)

(B) "Damaging" time curves: These curves are generally not available from the manufacturer, but they can be made up by applying a "factor of safety" to the melting time curves. For REA work, it is suggested that the curve be made by taking 75% of the melting time (in seconds) of a particular size for each current. For example, in Figure 1 below, if curve (1) represents the melting time characteristic for a certain size, curve (2) will represent the "damaging" time.

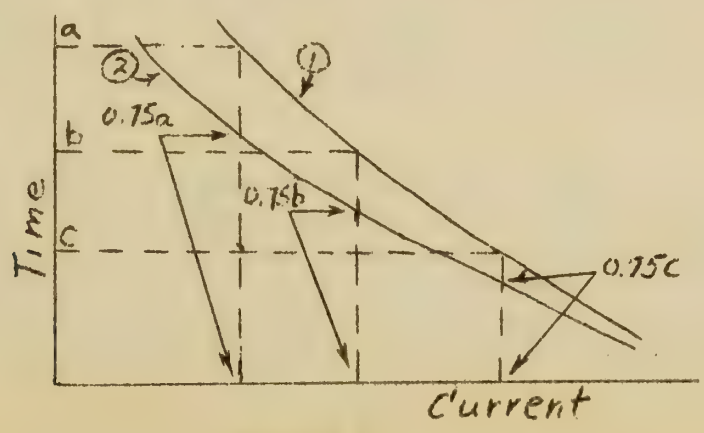

Figure 1.

These curves represent for each size the time in which a fuse will be damaged, or rendered unfit for further use by various fault currents.

If fusing tables such as on pages 57 & 58 are obtained, it is only necessary to plot damaging time curves for the fuse on the supply side of the substation. If such tables are not available, damaging time curves must also be made for the fuses on the load side. Total clearing time curves should be plotted or obtained for fuses on the load (REA) side in any case.

Some manufacturers make a fuse filled with powder which, it is said, aids in extinguishing the arc. In such cases, the "melting" time curve is generally called a "heating" time curve.

The next step is to select the fuse at the substation so as to protect the substation transformers against any fault current likely to occur.

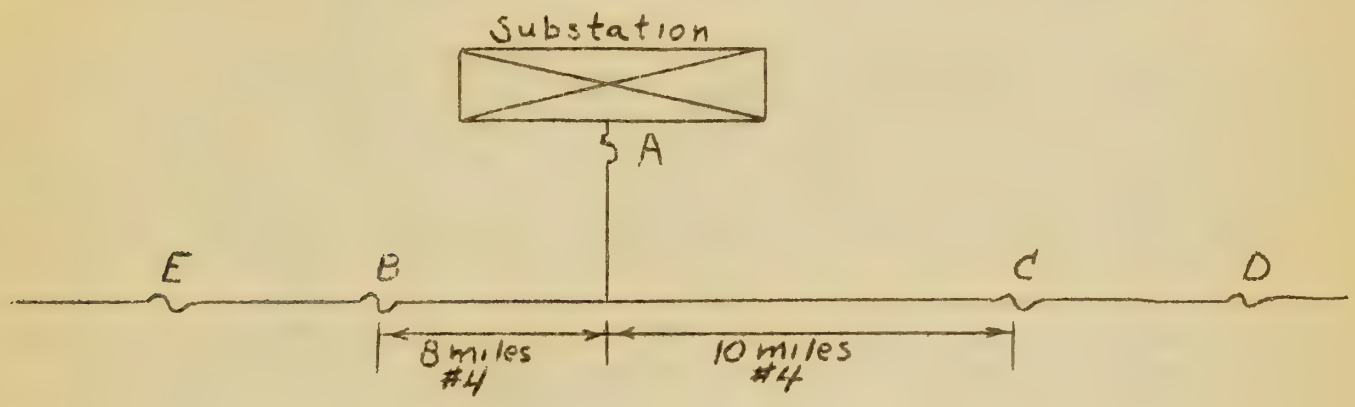

Figure 2.

Each fused device may be thought of as being in charge or control of all the line on the load side of the device up to the next device in series with it, in the direction away from the substation.

In Figure 2, the fuses at A must operate for fault current in its controlled section ABC before the substation transformers are damaged. Fuse B controls section EB, and fuse C controls section CD.

Due to the relative slopes of the transformer damage time curve and the fuse clearing time curve, the minimum current in the section under control is the one to be checked. (See Plate "F", page 64.) If the fuse protects the transformer for the minimum fault current, the fuse will also protect for any greater current. This is not necessarily true for circuit breakers.

Since point C is further from the substation than point B, in Figure 2, this means that with minimum fault current at point C, fuses at A must protect the substation against damage. The fuses at C are assumed to take care of faults beyond C. This minimum current may be either a line-to-ground, three phase, or line-to-line fault current.

Curve sheets 1A, 1B, and 1C, pages 39, 40 and 41, show the A.S.A. proposed curves for permissible short time overloads of transformers. Plot the curve of the particular substation transformer size used on the project, on the sheet of the total clearing time curves of the fuses used. Now on the current scale of these curves, find the minimum current at point C. Select a tentative fuse size rated at about double the capacity of the transformer bank.

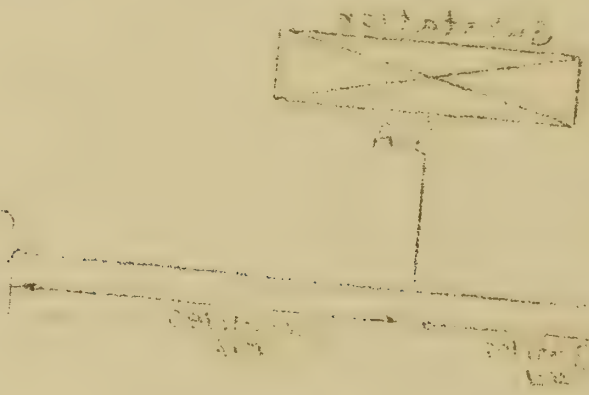

Figure 2.

For a single shot fuse at A for the above minimum current, if the total clearing time of the fuse is less than for damage of the transformer to occur, the fuse is safe. For a two-shot fuse, multiply the total clearing time of the fuse by two, and compare with the failure time of the transformers for the same current. If the total fuse time is lower, the fuse is safe. If higher, a lower rating must be used. For a three-shot fuse, multiply the clearing time by three, and proceed as above. If the first shot, or the first two shots, are tentatively to be fused at a lower value than the last, simply add the total clearing times of all two or three fuses for the particular minimum current and compare with the transformer damage time as before. The total clearing time of the substation fuses must be less than the time taken to damage the transformer on minimum fault current in the controlled section. This process neglects any cooling due to time-delay between shots, and is therefore conservative. In order to provide margin for sectionalizing on the remainder of the project, the fuses at the substation should be made as large as possible, while still maintaining safe protection of the substation.

It is practically impossible to protect the substation transformers against overload by the use of fuses, and still obtain the necessary number of sectionalizing steps on a project. A thermal indicator, either visual or with alarm system, can be used to indicate long-time overloads. Next, a check must be made to see that the substation fuse size so selected coordinates with the fuse or breaker on the supply side of the transformer. To obtain the fault current referred to the supply side, use formulas (13), (14) and (15).

I_L should be the maximum fault current right at the substation on the load (REA) side. Determine the total clearing time of the load side fuse at the maximum I_L (right at the REA side of the substation). If two-shot, multiply this time by 2, and if three-shot, multiply by 3. If different fuse sizes are used, add the total clearing times of the fuses in all shots. Compare this time with the damaging time (3/4 of the melting time) of the tentative fuse selected for the supply side at the I_s determined by (13), (14) and (15). If the time of the REA side fuses is less, the coordination is probably satisfactory. If more, either the REA fuse sizes must be reduced, or the supply side fuse size increased.

Since the characteristic of the supply side fuse link is different from that of the load side fuse link, coordination at maximum current may not necessarily indicate such coordination over the entire range of possible fault currents, although this is the usual case. To make such coordination certain, the complete characteristics should be plotted and compared. (See Plate "F", example.) Since the current conversion formulas indicate a much greater relative difference between load and supply currents for a line-to-line fault than for the other two types, the line-to-line fault current will usually be the criterion insofar as coordination between supply and load side devices is concerned. However, it will often be found that the supply side fuse is so limited in size by the supply organization that it is not possible to obtain coordination on this basis and still use the necessary devices on the REA lines. In this case, the three-phase fault, or line-to-ground fault conversion formula is used, and it is assumed that the supply fuse will blow for the occasional times that other types of faults occur.

Close cooperation with the power supply organization must be obtained in selecting the supply side fuse. No fuse should be selected without the supply organization's approval. If the substation is supplied by an REA plant, the supply side fuses must naturally be coordinated with any sectionalizing devices in the plant.

No account is taken above of the cooling effect due to time delay of the cut-out on the REA (load) side. No accurate method, short of actual test, can accomplish this. Judgment may be used on the part of the engineer in borderline cases. If there is a breaker on the supply side, the time of the load side fuses, as determined above, should be less than the first opening time of the breaker for the range of fault currents encountered. The breaker time or relay time can generally be obtained from the power supply organization.

The size of the fuses at the substation are now definitely known.

Now proceed to the last sectionalizing point on the system. On a distribution transformer failure, the fuse at this point should withstand the maximum short circuit current at this point while the transformer fuse blows. In other words, the last sectionalizing fuse should coordinate with the transformer cut-out fuse immediately beyond it. (For exceptions, read remainder of text.) The following table is recommended for distribution transformers.

Table

Transformer rating, KVA	$1\frac{1}{2}$	3	5	$7\frac{1}{2}$	10
Transformer Fuse rating, Amps	2	2	3	5	5

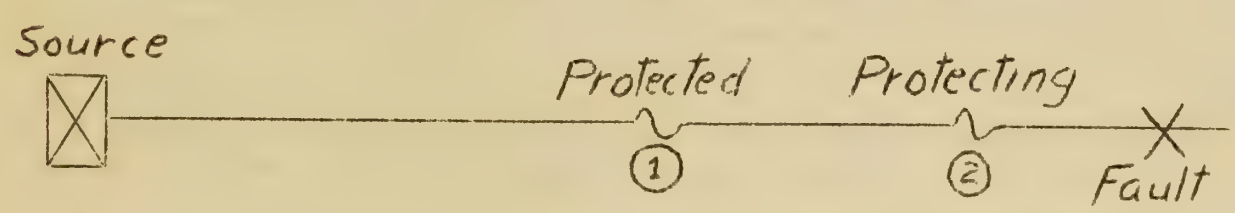

Figure 3.

Figure 3 illustrates the general principles of coordination. Fuse (1) is called the protected fuse and fuse (2) the protecting fuse. For perfect coordination, fuse (2) must clear the circuit on a fault anywhere beyond it (in the section controlled by fuse (2)) before fuse (1) is damaged. If (2) is a two-or three-shot, all two or three fuses should clear before any fuse at point 1 is damaged. For this reason it is more difficult to coordinate two- or three-shot fuses in the order named than single-shots.

Due to the inherent characteristics of fuses, the maximum current in the section controlled by fuse (2) is the determining current, which means the maximum fault current at point (2) should be used in coordinating the fuse links. This rule holds good only so long as the fuse links are of the same type. If links of different type or manufacture are used, coordination must be checked over the entire range of fault currents in the section controlled by fuse (2). (For example, load and power fuses at the substation.)

In case of the last line fuse on the system, point (1) represents the sectionalizing fuse, and point (2) the transformer fuse immediately beyond it.

Most fuse link manufacturers have now published tables which make such coordination very simple (see example for sample table). The values in the left hand column are the protecting fuse ratings (2) and the values across the top, the protected fuse ratings (1). The values in the table then show for what short circuit currents fuse (1) will be protected by fuse (2). These are maximum values; in other words, for any short circuit current greater than that shown, fuse (1) will be damaged, and hence a larger size must be used, or the position must be changed. The fault is assumed to occur just beyond position (2). For example, assume the maximum fault current at the last sectionalizing point is 40 amperes, and the distribution transformer cut-out fuse is rated 2 amperes. It can be seen from the sample table that a 5 ampere fuse will be "protected", by a 2 ampere fuse up to 60 amperes, and hence is satisfactory. A 3 ampere fuse is not satisfactory since no value is given in the table for a 2-3 combination. If the fault current were greater than 60 amperes, it would be necessary to go to an 8 ampere fuse on the line.

Now a check must be made to see that the 5 ampere fuse is not <u>too</u> large to blow under minimum fault current at the extreme end of the line. This is done by making sure that the minimum fault current is greater than the current to blow the fuse in 100 seconds. This can be obtained from the <u>total clearing time curves</u> of the fuse link used.

This check is important, and should always be made. Furthermore, in cases of long systems connected to small plants and substations, this check should be made for every line fuse on the system; i.e., each must blow on the <u>minimum</u> fault current at the next sectionalizing point, in other words, at the end of its controlled section. Ordinarily, the above checks are necessary at only one or two points, but if there is any reasonable doubt as to a fuse blowing, a check should be made in each case.

Assuming that the 5 ampere fuse is safe, this rating is now definite and the size of the next fuse toward the substation must be determined. The 5 ampere fuse now becomes the "protecting" fuse, and the next one toward the substation, the "protected" fuse. Here the same procedure is repeated as before. The protected fuse must withstand the maximum fault current at the position of the 5 ampere (protecting) fuse during the time the 5 ampere fuse is blowing. Assume this current is 60 amperes. It can be seen from the table that a 5 ampere fuse (left column) will protect a 10 ampere fuse up to 60 amperes. Hence, a 10 ampere fuse is satisfactory at the next point.

If a 5 ampere fuse is two-shot, however, it will be necessary to go to a 15 ampere fuse at the next point, as the table shows coordination only up to 25 amperes for a two-shot 5 ampere fuse with a 10 ampere fuse. If the 5 ampere fuse is used in a two-shot, the table shows a 15 ampere fuse in the next step will be satisfactory. Assuming a two-shot fuse, the 15 ampere size is selected, and now becomes the protecting position, and the next fuse in line becomes the "protected" position, and the process is repeated for the maximum fault current at the 15 ampere position.

This method of selection is continued until the substation fuse is reached. The size of this fuse has already been selected from other considerations, and the next fuse farther out must coordinate with the substation fuses. If the substation fuses are not large enough to withstand the maximum fault current at the next sectionalizing point farther out while the fuses at this point are blowing, then the size of the fuses at this sectionalizing point must be reduced. This may in turn necessitate any one of the following steps:

(1) Reduction of all fuse sizes, clear out to the end of the system.

(2) Replacement of some three-shot fuses by two-shots, and some two shots by single-shots.

(3) Elimination of one or more automatic sectionalizing points, replacing with non-automatic switches, if desired.

Whenever a branch line taps off the main line, and is fused, this fuse must be coordinated with the next fuse in the direction of the substation as before. Every line fuse should, if possible, coordinate with the primary transformer fuse next to it.

When internally fused transformers are used, it is usually difficult, if not impossible, to coordinate the line fuses near the ends of the lines with the internal transformer fuse, and still provide sufficient sectionalizing points on the system. In most cases, such transformers have secondary breakers, which render the situation less serious. However, in some cases, an interruption of service may be necessary until the damaged transformer is located.

Fuse curves can also be used for coordination in place of the tables. The method of coordination is to make sure that the total clearing time of the protecting link point (2) is less than the damaging time of the protected link point (1) for the maximum short circuit current at the position of the protecting link. For two- or three-shot fuses, the total clearing time of the protecting link must be multiplied by 2 or 3, if the reclosings are instantaneous, or by some lesser factors if there is time delay in reclosing. The tables, which are generally compiled from actual tests, take all these factors into consideration, and are hence much more accurate.

Expediencies:

In some cases, where an insufficient number of sectionalizing devices can be used, various methods can be used to install additional devices. For example, a single-shot 5 ampere fuse might have been used in the first position above instead of a two-shot. Then, a two-shot 5 or 8 ampere fuse could be used in the next position, and possibly a three-shot 5 or 8 ampere fuse in the next position toward the substation. By this means an additional device or two in series may often be added. This is purely an expediency, however, and should be used only as a last resort. Linemen must be instructed to replace all fuses at all of the two or three positions upon fault beyond the last one, as all fuses are likely to be damaged.

Sometimes, if perfect coordination of two or three shot fuses cannot be obtained, the best possible combination is recommended, with instructions to the project to not only replace the blown fuse links but also the first fuse link in the preceding cut-out toward the substation, even though this fuse link appears to be undamaged. In fact, the latter rule is a good one in any case.

Another aid in sectionalizing is to use a three-shot at the substation with the first cartridge fused light, and the others according to needs for coordination. Temporary trouble on the lines blows the first fuse, which is easily replaced, as it is generally near the office and hence saves a trip by the linemen. The first cartridge fuse must, of course, carry the load current.

Another method is to eliminate the distribution transformer cut-out fuse from consideration. In other words, the last sectionalizing fuse is made about the same size as the transformer fuse, or at times, even smaller, and is allowed to blow when the transformer fails. The method of operation when this occurs is to short out the line fuse with a jumper on a hot stick, thus burning out the transformer fuse or internal link and clearing the line. In this case, the next line sectionalizing device toward the substation must be made large enough to hold in while the transformer fuse blows. This method is generally more applicable with internally fused transformers, if the internal fuse rating is high.

Where the above method of shorting out the line sectionalizing device to blow the transformer weak link is used, a check should be made to see that there is sufficient minimum current to cause the weak link to melt.

VI. Coordination of Breakers and Reclosers

Breakers for REA lines may be placed in one of two classes: (A) magnetically operated; (B) operated by relay.

A. Magnetically Operated Breakers (opened by means of a coil)

Magnetically operated breakers are not subject to thermal limitations and hence breakers of this type reclosing two or more times may be coordinated with each other just as though they had only one opening. The method is to compare the first opening curves of the protected and protecting breaker. The time of opening of the protecting breaker must be less than the time of opening of the protected breaker for all ranges of fault currents to be expected.

It is necessary that there is sufficient minimum current at the end of each controlled section to operate the controlling breaker. For example in figure 4 there must be sufficient minimum current at the end of the section controlled by breaker (2) to provide pickup for breaker (2). The same applies to breaker (1). Furthermore, the control zones should overlap sufficiently so that there is no possibility of any section being unprotected. This can be accomplished by allowing ample margin between the minimum breaker pickup and the minimum current in the controlled section. The manufacturer supplies data in regard to minimum pickup. (See page 61)

This check is particularly important for this type of breaker. (This includes breakers such as the G.E. FP-119.)

In cases where breakers are used to protect a substation it is sometimes desirable to provide additional protection for the substation transformers for currents below the minimum trip current of the breaker. This may be done by checking the protection given by the supply side fuse, or if this is inadequate, a fuse may be installed between the breaker and the substation which will have a time-current characteristic greater than that of the breaker for the breaker operating range, but which will give additional protection for fault currents below which the breaker will not operate.

The above procedure may be unnecessary where the fault currents are more than ample to operate the breaker, but does offer a second line of defense in borderline cases. It is not possible, however, to give long time overload protection with such overcurrent devices.

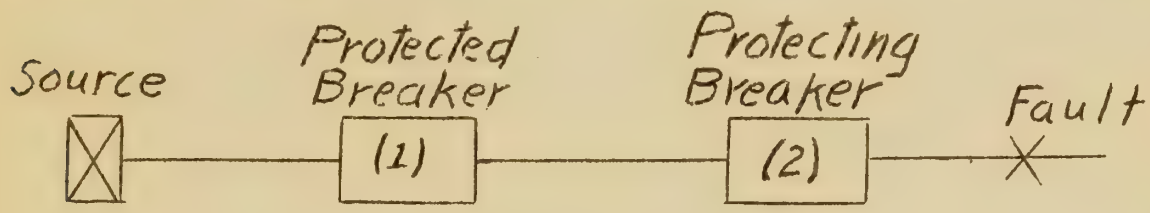

Figure 4.

Reclosing breakers can also be coordinated in some cases by varying the number of reclosings. For example, the protecting breaker can be made for two reclosures, and the protected breaker for three, etc. This method is not generally recommended, but may be used in occasional cases.

Breakers of all types can also be coordinated with fuses by comparing the proper characteristics. Magnetic breakers generally have an entirely different time-current characteristic than fuses, and hence are more difficult to coordinate than fuses alone.

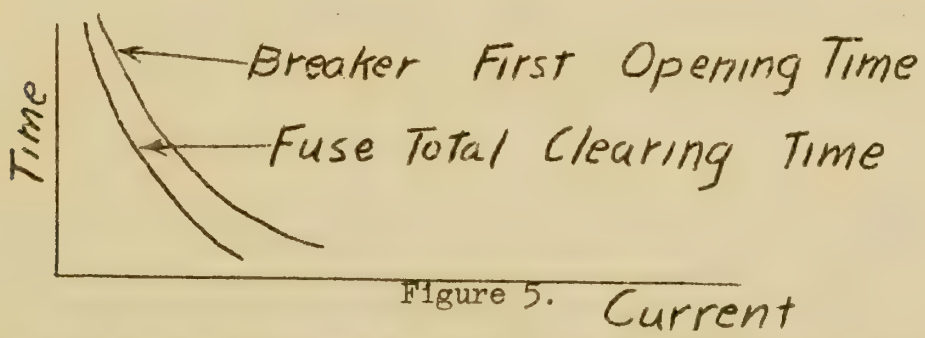

Figure 5.

If the fuse is protecting the breaker, the total clearing time fuse curve should lie entirely to the left of the first opening time curve of the breakers as in Figure 5. This is the condition which must be fulfilled where the transformer primaries are fused, or there are line fuses beyond the breaker. In some cases, if the breaker has three reclosings, and the fuse is a single-shot, the second opening time curve corrected for heating of the fuse may be used instead of the first (curves generally obtainable from the manufacturer.) (See page 62.) In other words, the breaker may

initially open before the fuse on a fault beyond the fuse, but the fuse is so heated that on the second reclosing of the breaker the fuse will immediately blow. This method should be used with discretion, however, and is obviously not so desirable if the fuse is a two-shot.

If the breaker is protecting a fuse, Figure 6 applies.

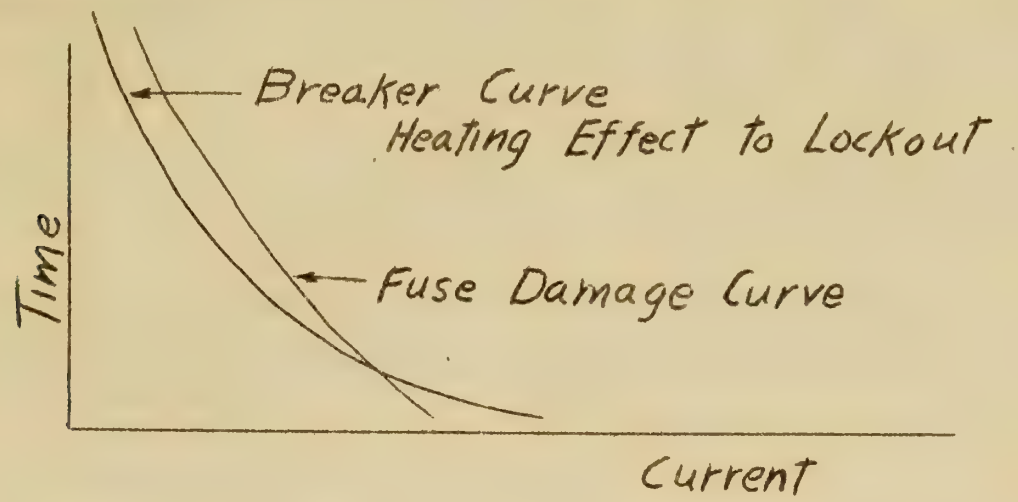

Figure 6.

The damaging time of the fuse for the range of short circuit currents expected must be greater than the time of the breaker, corrected to account for heating of the fuse during reclosures as in Figure 6. Most manufacturers will give these data. This is generally the case where a breaker is used on the load side of the substation, and a fuse on the supply side. The current passing through the supply side fuse must, of course, be obtained by correcting by the ratio of transformation as indicated above. If the breaker opens only once and does not reclose, the opening time curve may be used.

B. Relay-Operated Breakers

Breakers controlled by relays are used primarily in power plants supplying the project and occasionally at the substation. The most usual type is the overcurrent relay. In coordinating the relay, the time-current characteristics of the relay must be compared with the characteristics of the next device in series with it.

There are three general types of overcurrent relays in use: the solenoid plunger-type with and without time delay, and the induction type. For coordination purposes, it is preferable to have a relay with time-delay tripping, as otherwise the relay must be set very high to avoid improper operation. The solenoid plunger-type is usually used in small plants, and usually carries the total current. There is a calibrated set-screw or other device on the relay which determines its tripping current. The induction type, however, is almost always connected to the main circuit by means of a current transformer. In order to properly set the relay, it is therefore necessary to know the current transformer ratio.

The induction relay has two methods of adjustment: (1) by changing the current tap setting, and (2) by changing the time lever setting. The current tap setting determines the minimum "pickup" current point, while the time lever setting determines the amount of time delay in the tripping. The tripping characteristics are usually stamped on the face of the relay.

For example, suppose the current transformer ratio is 200 to 5 and the tap setting on the relay is 4 amperes. This means that the minimum closing current (100 percent point) is $\frac{200}{5}(4) = 160$ amperes. The relay field is too broad to cover in a short paper. Suffice to say that there are a large number of different types of relays. The general method in each case is to compare time-current characteristics for coordination purposes.

In protecting a substation transformer with a breaker of any kind, the entire relay curve should be plotted and compared with the transformer "damage" curve, as it is <u>not</u> sufficient to check the breaker for only minimum current in the controlled section.

VII. Current-Interrupting and Carrying Capacity

It is now necessary to see if the cut-outs or breakers are of sufficient capacity to interrupt the maximum fault current to be expected through each device. Cut-outs for 7200/12500-volt REA lines are specified to interrupt current as follows:

50 ampere rating - 1,200 amps.
100 ampere rating - 3,000 amps.

The interrupting rating of a breaker is usually stamped on the name plate or given in the data sheet. The interrupting check on a breaker is very important and must be made in each case. The fuse or other device on the supply side of the substation <u>must</u> be checked to see that it has sufficient capacity to interrupt the maximum fault current on the <u>supply</u> side. The manufacturer will furnish interrupting ratings.

<u>Current-Carrying Capacity</u>: Fuse links and breakers are also rated according to the continuous current carrying capacity. It is necessary to check the maximum <u>load</u> current passing through each fuse or breaker to see that it can safely and continuously carry that current. These loads have usually been determined in a previous voltage regulation study or if they have not, curve sheets 3a, 3b and 3c may be used in estimating the maximum load current. The safe current carrying capacity of a fuse is simply the value of the fuse size (i.e., 5 amps., etc.). It is also necessary to check the cut-out rating. For example, any fuse over a 50 ampere rating must be used in a 100 ampere cut-out. (Some manufacturers have special fuse ratings to avoid this.) The breaker rating is specified on the name plate.

To facilitate the work, the current carrying the interrupting ratings can be checked at the same time the coordination work is done, so that a fuse size or breaker selected for coordination can be immediately checked for proper current rating.

VIII. Sectionalizing in General

In making studies based on the use of different types of devices, a chart of the time-current characteristics is usually helpful as it shows the coordination visually. Log-log paper is the best. It is necessary to transfer all currents to a common base (usually 7200 volts) to show all relationships. The substation transformer damage time curve should also be shown. (See example, Plates "F" and "G", pages 64 and 65.)

A study of this type should always be made before purchasing additional sectionalizing devices, particularly expensive devices such as breakers. Promiscuous purchase of devices is dangerous and uneconomical.

In many cases, it may be impossible to obtain the desired number of automatic sectionalizing devices. In these cases, manually operated switches of one sort or other are effective. For the three-phase lines, it may be preferable to have a three-pole switch, operated from the ground. Single-phase lines can advantageously use inexpensive blade switches, disconnecting cut-outs, operated by hook stick, or hot line clamps. Use of such devices depends on the economic justification for them.

Where there are a number of three-phase motors on a project, either three-pole breakers should be used on the lines or each motor should be equipped with overcurrent protection on at least two phases of the starter, in order to prevent motor burn-up. In addition, the transformer bank should be connected with floating neutral (see Operations Memorandum #15.) Where distribution transformers on a tap are equipped with gaps instead of arresters, reclosing breakers must be used to control this tap, as fuses would blow too often due to gap operation.

In bad lightning areas, lightning may often be the cause of fuse or breaker outages. This is particularly true where there are no arresters for a mile or so on each side of the fuse. Often, on a three-phase or "V" circuit, no transformers, and hence no arresters, are connected to one or two of the phase wires at the position of the sectionalizing device. In such cases, the installation of an arrester near the device will quickly pay for itself in reduced outage time.

Adequate sectionalizing may very often raise a question as to the length of lines run from a single substation. With present devices, it is difficult to sectionalize properly with extremely long lines. In some cases the fault currents may be very low. Such considerations may point to the use of smaller units of line, fed from two or more substations, rather than large projects fed from a single source.

Such a question is, of course, tied up with the rate and power supply question, but sectionalizing problems may require serious consideration of alternate possibilities of power source.

IX. Completion of Work and Instructions to Project

After making all studies, and selecting fuse and breaker sizes, a complete map of the project should be prepared, with the selected apparatus and sizes clearly indicated. Several copies should be left with the project management and a copy sent to REA. Copies of all original data and calculations should also be left with the project.

The project should instruct its linemen to always replace a fuse by a link of the proper size and make. Linemen should have a copy of the sectionalizing map, and an ample stock of all sizes of links.

It should be understood that a theoretical study will not always give perfect results in practice. It may be necessary to change fuse link sizes, or move breakers, as dictated by experience. It is very dangerous, however, to increase fuse or breaker sizes just to keep from making trips. Rather the trouble should be cleared up at its source. A change in fuse size, or a breaker replacement or adjustment, should be made only by authorization of the superintendent or manager, after careful consideration and with conclusive evidence that the presently used sizes do not coordinate properly. Such changes should then be made on the map, and operation continued as before.

Fuse links may often be at the seat of difficulties on a project, and it may be necessary to try a different kind. If this is done, a re-study, using the new brand, should be made. Different makes of fuse links must not be mixed on lines receiving power from the same substation. If any change is made, it should be complete.

When any changes are made to the project, such as additions or revisions of line or increase in size of the substation, a supplementary study should be made to keep the sectionalizing program up to date.

No automatic devices should be purchased until it is certain that they will fit into the coordination scheme, and are economically feasible.

X. Protection of Distribution Transformers

Some of the points involving distribution transformer protection have already been sketchily outlined. This section will give a general method for more scientific methods of calculating proper size apparatus for such protection.

Transformers may be protected by devices on the primary, the secondary, or on both sides. Various devices, such as fuses or breakers, either internal or external, may be used. Some manufacturers make transformers with secondary breakers as an integral part of the transformer, and in such cases, the device is presumed to give adequate protection from faults or overloads on the secondary side. This discussion will not concern itself with such cases, as the setting of the breaker is fixed by the manufacturer. The service length, however, is the limiting factor in installations of this kind.

IX. Consolidation of Work and Instructions to Project

After making all studies, and selecting fuse and breaker sizes, a complete map of the project should be prepared, with the selected apparatus and wire sizes clearly indicated. Several copies should be left with the project management and a copy sent to RMA. Complete [illegible] weighted [illegible] should also be left with the [illegible]

A. Fused Protection

1. Primary side

Ordinarily, fuses can protect only against fault conditions on the secondary side. If the fuse is set so as to give protection against overload, it will be of such a low rating as to give too many false operations from other causes such as lightning, vibration, birds, or improper coordination with fuse and breaker ratings on the consumer's premises.

Curve sheets 2A and 2B, pages 42 & 43, give the fault current on the primary of the transformer for different size units and for different lengths of service line. These curves are based on a transformer impedance of 3.5%, which is generally greater than the impedance of those now in use, and hence the curves are conservative. Fault resistance and primary line impedance have not been considered in the curves on sheets 2A and 2B. Since both the transformer damage curves in sheet 1C and the 3.5% impedance value used are conservative, it is probably not necessary to add further safety factors for these other impedances. In fact, in some cases, the 3.5% impedance value may be somewhat too great, in which case the engineer can make up other curves based on a lower impedance value. For transformer impedances greater than 3.5%, the curves should be used with discretion.

If the primary fuse is to give protection for secondary faults, it must be selected so that it will clear the circuit on the minimum possible fault current before the transformer is damaged. It can be seen from curve sheets 2A and 2B that insofar as the primary fault current is concerned, a 120-volt secondary fault on a 3-wire 240/120-volt service gives the least primary fault current for any length service.

Suppose it is assumed that a 2-ampere Super #XX-1D fuse is to be used to protect a 5 kva 7200-240/120-volt transformer. The next question becomes: "What is the maximum length of service for which this fuse will give adequate protection to the transformer?".

Curve sheet 1C, page 41, gives the proposed A.S.A. standard for permissible emergency short time transformer overloads. As the transformer is connected for 3-wire service, each secondary winding is rated for only half capacity, and the primary rating, insofar as damage to the transformer is concerned on a 120-volt fault, is only half the 5 kva rating. Hence the primary current values on the damage curve are only half those of the regular 5 kva damage curve for the same time values. For a two-wire secondary (secondary coils in parallel) the full primary damage curve would be used. On plate "B", page 60, is plotted a short section of the damage curve (taken from curve sheet 1C of the 5 kva (3-wire) transformer.

1. Primary side

[illegible] fuses can protect only against [illegible] the primary side. If the fuse [illegible] is overload, it will [illegible] many false operations [illegible] lightning, birds, or transformer [illegible] faults on the consumer's premises.

[illegible] sheets 2A and 2B, pages [illegible] the primary of the transformer [illegible] not be under [illegible] proper coordinate of [illegible] the [illegible] of these [illegible] fault protection [illegible] in the primary [illegible] curve [illegible] protection [illegible] curve [illegible] the primary [illegible] curve should be used with [illegible].

If the primary fuse is to give protection for secondary [illegible] must be changed so that it will clear the [illegible] possible fault current before the transformer [illegible] is seen from curve sheet 2A and of that [illegible] fault current is approximately [illegible] 1.0 to 1.2 second [illegible] of 1.0 will generally [illegible] fourth position.

Suppose it is desired that [illegible] fuse is to be used to protect a 5 [illegible] chosen in beginning: [illegible] "Transformer" which this fuse will [illegible]

Curve sheet 1A, page 1A. [illegible] logically emphasize [illegible] the primary [illegible] only half [illegible] the [illegible] primary [illegible] on a [illegible] leave the primary [illegible] the [illegible] of the [illegible] two [illegible] damage [illegible] not [illegible]

It can be seen that it intersects the 2-ampere fuse curve at 13.3 seconds. From Curve sheet 1C at 13.3 seconds, we find a value of 11.1 times normal. In other words, for a primary current of less than 11.1 times normal, the transformer will be damaged before the fuse clears the circuit. Turning now to curve sheet 2A, we see that at 11.1 times normal primary current for a 120-volt fault on a 3-wire service, the service distance for a 5 kva 3.5% impedance transformer is 95 feet for a #8 service, 155 feet for a #6 service, and 240 feet for a #4 service. Any distances greater than these would be dangerous.

For 2-wire services, curve sheet 2B, page 43, is used, and the damage curve of the total transformer rating is applied. For example, suppose the question is as follows: Will a 2-ampere Super #XX-1D fuse protect a $1\frac{1}{2}$ kva transformer on a 200-foot 2-wire #6 service?

From curve sheet 2B we see that a 200-foot, 2-wire #6 service gives 19.15 times normal current on a $1\frac{1}{2}$ kva transformer. From curve sheet 1C the transformer will be damaged on a 19.15 times normal current in 5.9 seconds. The actual current on a 7200-volt base for the $1\frac{1}{2}$ kva size is 3.99 amperes. From Plate "B" the 2-ampere fuse will clear the circuit in 10 seconds on a fault of 3.99 amperes and hence will not protect the transformer.

2. Secondary Side

For secondary protection, the minimum fault current through the fuse may be either on a 120-volt or a 240-volt fault, depending on the service distance.

Suppose the question is as follows: For what service length will a 50-ampere Super #Y2-M2 secondary fuse protect a $1\frac{1}{2}$ kva transformer on a #6 3-wire service?

From Plate "E", page 63, showing the time-current characteristics of the Super #Y2-M2 fuse link, we see that the damage curve of the $1\frac{1}{2}$ kva 3-wire transformer (taken from curve sheet 1C) crosses the 50-ampere fuse curve at 107 amperes or 17.15 times normal. For any values less than this, the transformer will be damaged before the fuse clears. Going now to curve sheet 2A, we find that for a 120-volt fault, an 800-foot service gives 17.15 times normal secondary current, while for a 240-volt fault, a 1085-foot service gives the same value. Since the 800-foot service is the smaller, this is the limiting value, and is used. If we had selected some larger fuse, the 240-volt fault might cause the limiting fault current instead of the 120-volt fault.

Suppose the problem was as follows: Will a 60-ampere Super #Y2-M2 secondary fuse link protect a $1\frac{1}{2}$ kva 3-wire transformer with a service length of 300 feet of #8 conductor?

[illegible] Time Curve sheet 10 at 15.5 seconds. We find a value of 11.1 times normal. In other words, the primary current is less than 11 times normal, the transformer will be [illegible] before the fuse clears the circuit. Therefore [illegible] 2A, we see that at 11.1 times normal primary current [illegible] 150-volt fault on a 7-mile service, the service distance [illegible] 1½ kva 3.3% impedance transformer is 95 feet for [illegible] 195 feet for a 4/0 service, and 240 feet for a [illegible] distances greater than these would be dangerous.

For 5-mile services, curve sheet 2A, page 43, [illegible] [illegible] of the total transformer rating [illegible] [illegible] the question is as follows: [illegible] [illegible] 1½ kva transformer [illegible] [illegible] 2 [illegible] 2P we see that a 200-volt, 2-wire [illegible] [illegible] 10.15 times normal current on a 1½ kva transformer. The curve sheet 1C the transformer will be [illegible] 15 times normal current in 3.9 seconds. The actual current [illegible] would be for the 1½ kva size is 3.95 amperes. Thus [illegible] the 2-ampere fuse will clear the circuit in 10 seconds [illegible] fault [illegible] 3 [illegible] amperes and hence will not protect the transformer.

Secondary Side

For secondary protection, the minimum fault current through the fuse may be either on a 150-volt or a 240-volt circuit, depending on the service distance.

Suppose the question is as follows: [illegible] what service length will a 30-ampere Super ¾12-HP secondary fuse protect a 1½ kva transformer on a 240-volt [illegible]

From Table "E" page 14, showing a three-current [illegible] of the Super ¾12-HP fuse, 11 X, we find that the lowest value of the 1½ kva 3-wire transformer (taken from curve sheet 1A) exceeds the 30-ampere fuse curve at 1.4 times normal. For any values less than this, the transformer will be damaged before the fuse clears. Using curve [illegible] 2A, we find that on a 1.4 X fault [illegible] 2-foot service wires, 12.4 times normal secondary current, which is the 1.4-X fault, [illegible] the 30-foot service is the same value. Since the 30-foot service is the minimum, this is the limiting [illegible] [illegible] service. [illegible] 1½ kva 3-wire transformer [illegible] fuse, the limit [illegible] [illegible] 240-volt [illegible]

[illegible] the curve sheet [illegible] 240-volt [illegible] [illegible] 1½ kva [illegible] [illegible] 2 [illegible] 2P feet [illegible]

From curve sheet 2A, we see that a 240-volt fault gives 22.4 times normal secondary current, while a 120-volt fault gives 23 times normal. Since the 240-volt fault gives the lower value, we test with it. On curve sheet 1C at 22.4 times normal current, the time for transformer damage is 4.7 seconds. At 22.4 times normal (140 amperes) on Plate "E" the 60-ampere fuse will blow in 1.15 seconds. Hence the fuse is safe.

On any particular job, the engineer, knowing the kind and size of secondary fuse to be used, can easily make up tables of maximum service length distances for safe protection. Such tables can then be given as instructions to the stakers. Similar tables can also be made for primary protection.

3. Primary and Secondary Protection

Where the transformer has both primary and secondary protection, the secondary device is assumed to take care of secondary faults, while the primary fuse is only for the purpose of removing the transformer from the line in event of failure.

B. Breaker Protection

Breaker sizes or service line lengths can be calculated in much the same manner as fuses. It is only necessary to have the tripping characteristics of the breaker instead of the clearing characteristics of the fuse.

C. Coordination of Secondary Fuse with House Fuse or Breaker, and with the Primary Transformer Fuse

It is necessary not only to select the proper fuse or breaker to protect the transformer if secondary protection is desired, but this fuse must be coordinated with the fuse or breaker in the house, and with the primary fuse, either internal or external, in the transformer. The methods used are exactly similar to those given above for sectionalizing. The clearing time of the house fuse or breaker must be less than the damaging time of the secondary fuse or breaker on the maximum fault current at the house fuse. The secondary fuse or breaker must clear the circuit in less time than taken to damage the internal or external primary fuse on the maximum fault current at the transformer terminals.

Curve sheets 2A and 2B will give the secondary fault currents. If the transformer impedance is materially less than 3.5%, this value should be increased. Characteristic time-current curves of the protective devices can be obtained from the manufacturers.

The following tables give primary and secondary fault currents for different transformer impedances for a fault on the transformer terminals. Use the percent transformer impedance nearest to that of those used on the project.

From curve sheet 2A, we see that a [illegible] gives 22 times normal secondary current, while a [illegible] fault gives 22 times normal. Since the [illegible] gives the lower value, we test with it. On curve sheet [illegible] 22.4 times normal current, the time [illegible] 4. [illegible] At 22.4 times normal (the current in [illegible] "B" the [illegible] fuse will blow in [illegible] sec. [illegible]. Hence the fuse [illegible].

On any part [illegible], the equipment, [illegible] rise of secondary [illegible] to be used, can be [illegible] as a guide of maximum [illegible] distances [illegible]. [illegible] can then be given as a [illegible] to the attendant. [illegible] can also [illegible] for ordinary [illegible].

[illegible] Secondary [illegible]

When the transformer has both primary and secondary [illegible], the secondary [illegible] to take care of secondary [illegible], while the primary fuse is only for the purpose of removing the [illegible] from the line in event of failure.

Magnetic Protection

[illegible] either on service [illegible] be [illegible] to [illegible] [illegible] or three. [illegible] [illegible] the [illegible] [illegible] of the breaker [illegible] of the [illegible] of the fuse.

Coordination of Secondary Fuse with Primary Fuse or Breaker, [illegible] with the Primary Transformer Fuse

It is necessary not only to select the proper fuse or breaker [illegible] the transformer if secondary protection is desired, but [illegible] be coordinated with the fuse [illegible] in the house [illegible] primary fuse, either [illegible] the fuse. The methods used are exactly [illegible] shown for [illegible]. The [illegible] character [illegible] of the fuse [illegible] must be [illegible] the same [illegible] of the secondary [illegible] on the maximum fault current at the primary fuse. [illegible] secondary [illegible] the primary fuse blows [illegible] the internal [illegible] of primary fuse on the maximum [illegible] current at the transformer terminals.

Curve sheets 2A and 2B will give the secondary fault current [illegible]. In the transformer impedance is [illegible] then 3.5%, this value should be increased. Since [illegible] time-current curves of the protective devices can be obtained from the manufacturers.

[illegible] following table gives primary and secondary fault currents [illegible] transformer [illegible] a fault on the transformer [illegible] current transformer [illegible] that [illegible] [illegible].

PRIMARY AND SECONDARY FAULT CURRENTS
7200 VOLT PRIMARY 240/120 VOLT SECONDARY

TRANSFORMER PERCENT IMPEDANCE

120-VOLT FAULT ON THREE-WIRE SERVICE

Transf. KVA	2.00%		2.5%		3.00%		3.5%		4.00%	
	Pri.	Sec.	Pri.	Sec.	Pri.	Sec.	Pri.	Sec.	Pri.	Sec.
1.5	7.84	470	6.28	377	5.24	314	4.47	268	3.92	235
3	15.7	943	12.5	751	10.45	628	8.94	537	7.84	471
5	26.1	1570	20.9	1255	17.40	1045	14.9	895	13.05	784
7.5	39.2	2350	31.4	1885	26.20	1570	22.4	1345	19.60	1178
10	52.2	3140	41.8	2510	34.8	2090	29.7	1780	26.1	1570
240-VOLT FAULT ON THREE-WIRE SERVICE										
1.5	10.4	312	8.34	250	6.95	208	5.95	179	5.21	156
3	20.8	625	16.7	500	13.9	417	11.90	357	10.4	312
5	34.7	1042	27.8	834	23.1	694	19.8	595	17.4	522
7.5	52.1	1562	41.6	1250	34.7	1040	29.8	894	26.1	782
10	69.4	2080	55.5	1667	46.3	1390	39.7	1190	34.7	1040
120-VOLT FAULT ON TWO-WIRE SERVICE										
1.5	10.4	625	8.34	500	6.95	417	5.95	357	5.2	312
3	20.8	1250	16.7	1000	13.9	833	11.9	714	10.4	625
5	34.7	2085	27.8	1667	23.1	1388	19.8	1190	17.4	1042
7.5	52.1	3125	41.6	2500	34.7	2080	29.8	1786	26.1	1562
10	69.4	4160	55.5	3333	46.3	2780	39.7	5380	34.7	2080

Note: The transformer impedance is increased about 33% for a 120 V fault on a three wire service

Summary of Steps in Sectionalizing

XI.

A. Obtain complete data on the project and on the proposed devices before starting a study.

B. After study of the lines, both on the map and in the field, and talks with the operating personnel, make a tentative location of the sectionalizing devices.

C. Calculate maximum and minimum fault currents at each sectionalizing point, and at the ends of the lines. Calculate line-to-ground, three phase, and line-to-line faults.

D. Select the devices at the substation to give complete and adequate protection to the substation transformers from fault currents on the lines.

E. Coordinate the sectionalizing devices from the substation out, or from the ends back to the substation. Revise the tentative locations if necessary.

F. Check the selected devices for carrying and interrupting rating.

G. Prepare written instructions and a map for the operating personnel of the project.

H. Work out instructions to the project for service lengths on various sized distribution transformers.

Form TS-5
4-15-41

DEPARTMENT OF AGRICULTURE
RURAL ELECTRIFICATION ADMINISTRATION

TECHNICAL STANDARDS DIVISION

DATA REQUIRED FOR COMPLETE SECTIONALIZING STUDY
(Omission of any item will handicap our study)

I. Map of entire system (Send two copies.)
   A. Type
      1. Complete system on one sheet.
      2. Scale - Any key map will serve, but preferably about one-half inch to the mile. Be sure to show the scale on the map.
   B. Details to be shown
      1. Lines
         a. Location
         b. Kind of conductor (A.C.S.R., CWLD., Copper, etc.)
         c. Sizes of conductors (A.W.G.)
         d. Number of phases (1, 2 or 3) (Preferably shown by coloring - green for 3 phase, yellow for V circuit, and red for single phase.)
         e. Phase designation. Mark lines to indicate whether phase A, B or C, or give combination.
      2. Substations
         a. Location (If more than 1, number so as to correlate with diagrams under items IIA and IIB.)
      3. Source of Power
         If the power source is near the substation, indicate the location of the plant. If not, indicate the transmission system from which power is obtained.
      4. Fused cutouts on Lines (Do not show transformer cutouts.)
         a. Location
         b. Type (3-shot, 2-shot, 1-shot, or liquid fuse)
         c. Fuse link rating used at present.
      5. Breakers
         a. Location
         b. Rating
      6. Transformers
         If there are any transformers protected by gaps instead of arresters, show where these are located.
      7. Indicate the location of any consumer to whom a lengthy power interruption would be costly and detrimental.

II. Substation Information
   A. Diagram of Substation
      Show transformers, all outgoing lines at the substation and within one mile of it, and the location of every sectionalizing device on these lines. This should be a sketch not to scale. (See back page for sample.)
   B. Other Data (Obtain from transformer nameplate.)
      1. Capacity each transformer, KVA_____
      2. Percent reactance each transformer_____
      3. Percent resistance each transformer_____
      4. Percent impedance each transformer_____
      (If single 3-phase transformer is used, give above data per phase.)
      5. Exact voltage, line to line, supply side_____
      6. Exact voltage, line to ground, REA side_____
      (If there is more than one substation, number the diagram and other data to correspond with I B 2, above.)

III. Information Concerning Power Supply
(Answer A or B, depending on source.)

A. Private Utility or large municipal plant
(Obtain this data from the power source organization.)

1. Name of Utility _____
   Address _____

2. Fault Table

Line to Line Voltage at Substation _____	Short circuit currents at Substation under normal operating schedule	
	Maximum	Minimum
Line to line fault current, Amps.		
Line to ground fault current, Amps.		
Three-Phase fault current, Amps.		

3. Power Company Requirements
   What is the maximum size fuse (of same make as now used) or breaker current setting which the power supply organization will allow at the supply side of the substation? If a relay operates the breaker, give the maximum tap and time lever settings allowed. (See also IV.) Detail _____

B. Small Utility or Municipal Plant, or REA Power House

1. Name of organization supplying power _____
   Address _____
2. Give distance between the substation and the power house in miles.
3. Size and kind of conductor between the substation and this plant.
4. Plant data

a. Unit No.	Prime Mover Reciprocating Engine Turbine, or Diesel?	R. P. M.	Generator		
			Kva Capacity	Manufac-turer	Serial Number
1					
2					
3					
4					
5					

   b. Units running under normal Operation Schedule
      1. During minimum load _____
      2. During maximum load _____
   c. Line to line Voltage _____

5. What is the maximum size fuse (of same make as now used) or breaker current setting which this organization will allow at the supply side of the substation? If a relay operates the breaker, give the maximum tap and time lever settings allowed. (See also IV.) Detail _____

6. Diagram of Power House
   Indicate on a single line diagram all generators, main lines, and circuit breaker controlling the REA feeder. Number the machines and breakers to correspond with numbers given in data above. (See back page for sample.)

IV. Equipment Information

A. Circuit Breakers and Control

Location:-	Line	Substation Load Side	Substation Supply Side	Feeder in** Power Plant	Other (Specify)
Breaker Manufacturer					
Breaker Type or Style No.***					
Current time-delay dashpot (yes or no)					
Present Current Trip setting					
Control-Relay Manufacturer	1*				
	2*				
Control Relay Type or Style No.	1*				
	2*				
Present Relay Tap Setting	1*				
	2*				
Present Relay Time Lever Setting	1*				
	2*				
Relay Current Transformer Ratio	1*				
	2*				
Other Details (Specify)					

If no breakers are in use, write "none."

* If more than one type of relay controls the breaker (as overcurrent and ground), separate these on lines 1 and 2 for all items. If no relay is used, put none in proper space.

** Fill in this column only if receiving power from REA plant, municipal plant, or small utility.

*** Number on breaker tank.

B. Fuse Links

Location:-	Distribution Transformer	Line Sectionalizing	Substation-Load Side	Substation-Supply Side
Fuse Manufacturer				
Catalog or Style No.				

(List here the fuses which you would like to have standardized on your project.)

V. Description of Difficulties

A. Describe in detail on the reverse side what difficulties have been experienced with your present sectionalizing arrangement.

SAMPLE DIAGRAMS

(1) SUBSTATION SKETCH DIAGRAM

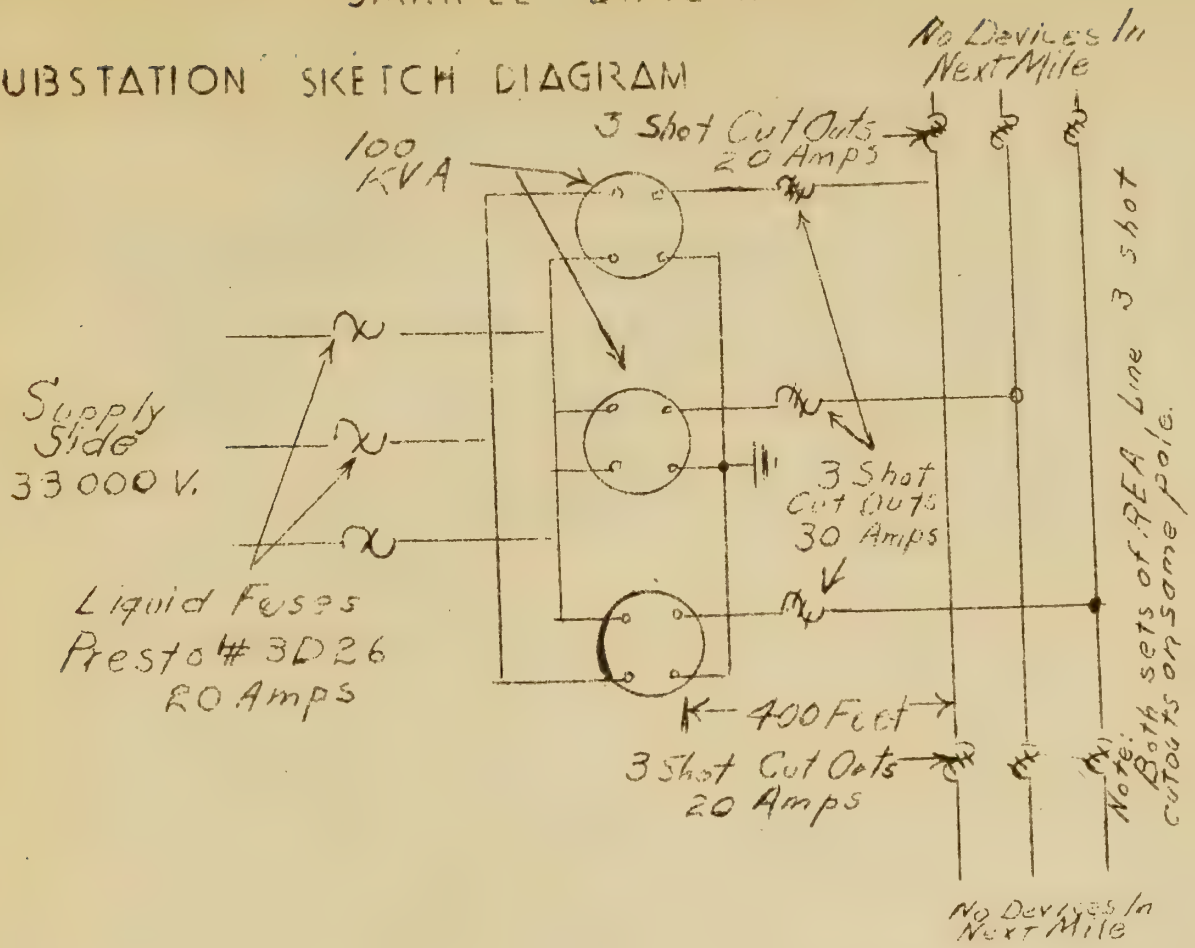

SUBSTATION FOR KANSAS 87 JONES

(2) POWER PLANT SKETCH DIAGRAM

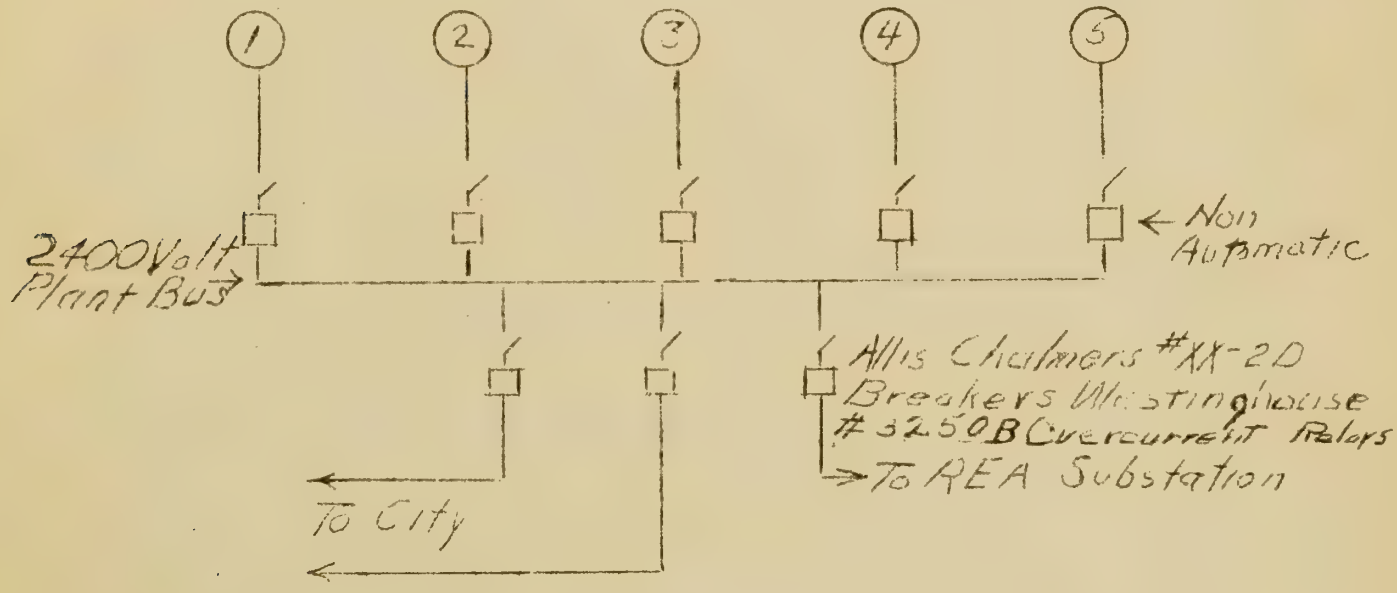

CATHAY MUNICIPAL PLANT

4961A

Appendix

Handy Formulas for Fault Calculations

A. <u>Impedance of REA Lines</u> (60 cycles) per mile

$$Z_g = r_c + 0.0954 + j0.2794 \log_{10} \frac{D_e}{R}$$

$$Z_{gm} = 0.0954 + j0.2794 \log_{10} \frac{D_e}{dab}$$

where Z_g = self-impedance of conductor

Z_{gm} = mutual impedance

r_c = resistance of conductor

$D_e = 2160\sqrt{\frac{p}{f}}$

p = ground resistivity ohms per cubic meter.

f = frequency (60)

R = geometric mean radius of conductor

dab = distance between conductors a and b (or geometric mean distance between conductor a and conductor group b)

For two wire single phase, thoroughly grounded neutral circuit.

$$Z_L = \left(Z_{aa} - \frac{Z_{an}^2}{Z_{nn}}\right)$$

where Z_L = Impedance of circuit

Z_{aa} = Self impedance of phase conductor

Z_{nn} = Self impedance of neutral conductor

Z_{an} = Mutual Impedance of phase or neutral conductor

For two-phase wires and neutral ("V" circuit)

$$Z_a = \left(Z_{aa} - \frac{(Z_{an})^2}{Z_{nn}}\right) + \frac{I_b}{I_a}\left(Z_{ab} - \frac{Z_{an}\, Z_{bn}}{Z_{nn}}\right)$$

$$Z_b = \left(Z_{bb} - \frac{(Z_{bn})^2}{Z_{nn}}\right) + \frac{I_a}{I_b}\left(Z_{ab} - \frac{Z_{an}\ Z_{bn}}{Z_{nn}}\right)$$

where I_a and I_b are equal and 120° apart,

$$Z_a = Z_1 - \frac{Z_2^2}{Z_{nn}}\ (1 + a^2) + a^2\ Z_{ab}$$

$$Z_b = Z_1 - \frac{Z_2^2}{Z_{nn}}\ (1 + a) + a\ Z_{ab}$$

where $Z_1 = Z_{aa} = Z_{bb}$

$Z_2 = Z_{an} = Z_{bn}$

$a = -0.5 + j0.866$

For three-phase wires and neutral

Assume balanced conditions (no ground current).

$$Z_L = r_c + j0.2794 \log_{10} \frac{G.M.D.}{R}$$

where Z_L = impedance of circuit

r_c = resistance of conductor

G.M.D. = geometric mean spacing

$= (\sqrt[3]{D_1 D_2 D_3}$ for 3 conductors)

R = geometric mean radius of conductor

Values of R for various conductors are shown on page 34.

$$u = -4 \log_e \frac{(R)}{(r)} = -9.210 \log_{10} \frac{(R)}{(r)}$$

where u = permeability

R = geometric mean radius

r = conductor radius (actual)

B. Formulas for fault currents

(1) 3-phase fault.

$$I_a = I_b = I_c \frac{E}{(Z_1) + Z_f}$$

[illegible]

$$Z_b = \left(Z_{1b} - \frac{(Z_{1m})^2}{Z_m}\right) + \frac{L_b}{L_1}\left(Z_{mb} - \frac{Z_{1m}\,Z_{bm}}{Z_m}\right)$$

[illegible] L_b are given [illegible] 100' apart.

Z_1 [illegible] $= 8^2$ [illegible]

$$Z_b = Z_1 - \frac{[illegible]}{Z_m} \quad [illegible]$$

where $Z_1 = [illegible] = Z_m$

[illegible]

where Z_b = impedance of [illegible]

r_o = radius [illegible]

G.M.D. = geometric mean spacing

$= \sqrt[3]{D_1 D_2 D_3}$ for [illegible]

[illegible] geometric mean radius [illegible]

Value of [illegible] for various conductors [illegible]

$$x = -4 \log_e \frac{(G)}{(r)} = -9.210 \log_{10} (r)$$

where [illegible] permeability

R = [illegible] in a radius

[illegible] mean radius (1 unit)

R_1 [illegible]

(1 [illegible] unit).

$$Z_b = [illegible] \ln \frac{(D_1)}{[illegible]} + [illegible]$$

(2) Line-to-ground fault

$$I_a = \frac{E}{\left(\frac{Z_1 + Z_2 + Z_0}{3}\right) + Z_f}$$

$$I_b = I_c = 0$$

(3) Line-to-line fault

$$I_a = 0$$

$$I_a = - I_b = \frac{j\sqrt{3}\ E}{(Z_1 + Z_2) + Z_f}$$

where

E = Line to ground voltage

Z_1 = Positive phase sequence impedance

Z_2 = Negative phase sequence impedance

Z_0 = Zero phase sequence impedance

Z_f = Fault impedance

I_a, I_b, I_c, currents in a, b and c phases.

C. Delta-Wye transformer bank current conversion formulas.

(1) 3-phase fault

$$I_{sa} = I_{sb} = I_{sc} = \sqrt{3} \quad (N) \quad (I_L)$$

(2) Line-to-ground fault

$$I_{sa} = I_{sb} = (N) \quad (I_L)$$

$$I_{sc} = 0$$

(3) Line-to-line fault

$$I_{sa} = 2(N) \quad (I_L)$$

$$I_{sb} = I_{sc} = (N) \quad (I_L)$$

where

I_{sa}, I_{sb}, I_{sc}, Line current in phases a, b and c on delta (supply) side.

I_L = fault current on wye (load) side.

N = Transformer turns ratio

$= \left(\frac{E_L}{E_s\ (L\text{-}L)} \quad \text{for delta-wye bank} \right)$

D. Decrement of positive sequence current in alternators.

$T_d' = \frac{X_d'}{X_d}\ (T_{do})$ for circuit having negligible resistance

$T_d' = \frac{X_d'\ X_q + r^2}{X_d\ X_q + r^2}\ T_{do}$ for circuit with resistance

where T_d' = transient time constant

X_d' = direct axis transient reactance (including line and machine)

X_q = quadrature axis synchronous reactance.

X_d = direct axis synchronous reactance (including machine and line)

r = resistance of machine and line.

T_{do} = open circuit time constant.

Then $I' = (I_i' - I)(e)^{\left(\frac{-t}{T_d'}\right)} + I$

where

I' = positive sequence transient current at anytime

I_i' = initial transient current

I = sustained short circuit current (from synchronous impedance)

e = 2.7183

(This neglects the subtransient value and the action of the voltage regulator)

E. Percent and per unit formulas.

$(\%\ \text{impedance}) = \frac{\text{ohms}\ (\text{KVA})}{(\text{KV})^2(10)}$

$\text{ohms} = \frac{(\%\ \text{impedance})\ \ (\text{KV})^2(10)}{\text{KVA}}$

If KVA is per phase, KV must be the line-to-ground value.
If KVA is total, KV must be the line-to-line value.

$\text{per unit impedance} = \frac{\text{percent impedance}}{100}$

[illegible]

I_f = fault current [illegible]

V = line-to-neutral voltage [illegible]

Z_f = fault impedance [illegible]

Z_1 = positive sequence [illegible]

Z_2 = negative sequence [illegible]

Z_0 = zero sequence [illegible]

Z_n = impedance [illegible]

Z_{1f} = [illegible] impedance (including [illegible])

X_1 = [illegible] reactance

X_2 = [illegible] reactance (i.e. [illegible] and line)

X_0 = [illegible] of positive sequence [illegible]

Z_{0f} = zero sequence with resistance.

Then $I_f = (Z_{1f} + Z_{2f} + Z_{0f})^{-1}$

where

Z_{1f} = positive sequence [illegible] current at the fault

Z_{2f} = negative sequence [illegible] current

Z_{0f} = zero sequence [illegible] fault current (from zero sequence impedance)

[illegible]

[illegible] substantiate the substantiate value and the action of the [illegible]

[illegible] and [illegible] reactance.

[illegible]

[illegible]

If XVA is per phase, KV must be the line-to-ground value.
If XVA is total, KV must be the line-to-line value.

[illegible] impedance = percent impedance / 100

To convert ohmic values from one voltage base to another, multiply by the square of the ratio of the line-to-ground voltages. (See above formulas.)

Geometric Mean Radius of Conductors

Solid round conductor	0.779 r
Full stranding, non-magnetic	
7 strands	0.726 r
19 strands	0.758 r
where r = $\frac{1}{2}$ of actual conductor diameter	
Rectangular section of sides a and b	0.2235(a + b)

A.C.S.R. conductors

2/0	0.0612 inches
1/0	0.0535 "
1	0.0502 "
2	0.0502 "
4	0.0523 "

Copper - Copperweld Conductors

Strands	Conductor	
7	7 copperweld	0.223 r
7	3 copperweld, 4 copper	0.3165 r
1	Solid copperweld	0.287 r
3	Type A, 1 copperweld, 2 copper	0.333 r
3	Type D, 2 copperweld, 1 copper	0.242 r
19	7 copperweld, 12 copper	0.564 r
3	3 copperweld	0.223 r

where r = $\frac{1}{2}$ actual conductor diameter

Feb. 1941

U.S. DEPARTMENT OF AGRICULTURE

Table I

RURAL ELECTRIFICATION ADMINISTRATION

AVERAGE R.E.A. SINGLE PHASE LINE IMPEDANCE FOR MULTI—GROUNDED LINES

EARTH RESISTIVITY EQUALS 100 METER OHMS

MILES	CONDUCTOR COPPER EQUIVALENT SIZE													
	1/0		2		4		6		8		9½		11	
	R_L	X_L	R_L	X_L	R_L	X_L	R_L	X_L	R_L	X_L	R_L	X_L	R_L	X_L
1	0.723	1.124	1.00	1.22	1.63	1.31	2.45	1.46	3.74	1.55	5.04	1.67	7.36	1.704
2	1.45	2.25	2.00	2.44	3.26	2.62	4.90	2.92	7.48	3.10	10.08	3.34	14.72	3.41
3	2.17	3.37	3.00	3.66	4.89	3.93	7.35	4.38	11.22	4.65	15.12	5.01	22.08	5.11
4	2.89	4.50	4.00	4.88	6.52	5.24	9.80	5.84	14.96	6.20	20.16	6.68	29.44	6.82
5	3.61	5.62	5.00	6.10	8.15	6.55	12.25	7.30	18.70	7.75	25.20	8.35	36.80	8.52
6	4.34	6.74	6.00	7.32	9.78	7.86	14.70	8.76	22.44	9.30	30.24	10.02	44.16	10.22
7	5.06	7.87	7.00	8.54	11.41	9.17	17.15	10.22	26.18	10.85	35.28	11.69	51.52	11.93
8	5.78	8.99	8.00	9.76	13.04	10.48	19.60	11.68	29.92	12.40	40.32	13.36	58.88	13.63
9	6.51	10.11	9.00	10.98	14.67	11.79	22.05	13.14	33.66	13.95	45.36	15.03	66.24	15.34
10	7.23	11.24	10.00	12.20	16.30	13.10	24.50	14.60	37.40	15.50	50.40	16.70	73.60	17.04
11	7.95	12.36	11.00	13.42	17.93	14.41	26.95	16.06	41.14	17.05	55.44	18.37	80.96	18.74
12	8.68	13.48	12.00	14.64	19.56	15.72	29.40	17.52	44.88	18.60	60.48	20.04	88.32	20.45
13	9.40	14.61	13.00	15.86	21.19	17.03	31.85	18.98	48.62	20.15	65.52	21.71	95.68	22.15
14	10.12	15.72	14.00	17.08	22.82	18.34	34.30	20.44	52.36	21.70	70.56	23.38	103.04	23.86
15	10.85	16.86	15.00	18.30	24.45	19.65	36.75	21.90	56.10	23.25	75.60	25.05	110.40	25.56
16	11.57	17.98	16.00	19.52	26.08	20.96	39.20	23.36	59.84	24.80	80.64	26.72	117.76	27.26
17	12.29	19.11	17.00	20.74	27.71	22.27	41.65	24.82	63.59	26.35	85.68	28.39	125.12	28.97
18	13.01	20.23	18.00	21.96	29.34	23.58	44.10	26.28	67.32	27.90	90.72	30.06	132.48	30.67
19	13.74	21.35	19.00	23.18	30.97	24.89	46.55	27.74	71.06	29.45	95.76	31.73	139.84	32.38
20	14.46	22.48	20.00	24.40	32.60	26.20	49.00	29.20	74.80	31.00	100.80	33.40	147.20	34.08
21	15.18	23.60	21.00	25.62	34.23	27.51	51.45	30.66	78.54	32.55	105.84	35.07	154.56	35.78
22	15.91	24.73	22.00	26.84	35.86	28.82	53.90	32.12	82.28	34.10	110.88	36.74	161.92	37.49
23	16.63	25.85	23.00	28.06	37.49	30.13	56.35	33.58	86.02	35.65	115.92	38.41	169.28	39.19
24	17.35	26.98	24.00	29.28	39.12	31.44	58.80	35.04	89.76	37.20	120.96	40.08	176.64	40.90
25	18.08	28.10	25.00	30.50	40.75	32.75	61.25	36.50	93.50	38.75	126.00	41.75	184.00	42.60

Feb. 1941 | U.S. DEPARTMENT OF AGRICULTURE | Table II

RURAL ELECTRIFICATION ADMINISTRATION

IMPEDANCE OF R.E.A. LINES

OHMS PER CIRCUIT MILE

STANDARD R.E.A. SPACING:— *EARTH RESISTIVITY = 100 METER-OHMS*

WIRE SIZE	IMPEDANCE TO POSITIVE OR NEGATIVE SEQUENCE CURRENT 3 Ø LINES		SINGLE PHASE IMPEDANCE WITH MULTI-GROUNDED NEUTRAL WIRE		
	$R_1 = R_2$	$X_1 = X_2$	R	X	Z
COPPER CONDUCTORS — 20° C.					
1/0	0.551	0.734	—	—	—
1	0.694	0.748	—	—	—
2	0.867	0.759	0.998	1.225	1.580
4	1.369	0.797	1.605	1.311	2.073
6	2.170	0.825	2.417	1.424	2.805
COPPERWELD — COPPER CONDUCTORS — 20° C.					
6A	2.195	0.885	2.433	1.488	2.852
6A	3.480	0.901	3.706	1.577	4.028
9½D	—	—	5.040	1.666	5.308
3 12	—	—	7.357	1.704	7.552
A.C.S.R. CONDUCTORS — 25° C.					
3/0	0.561	0.732	—	—	—
2/0	0.707	0.745	—	—	—
1/0	0.889	0.748	1.099	1.200	1.628
2	1.410	0.781	1.653	1.300	2.103
4	2.240	0.804	2.490	1.409	2.860
6	3.560	0.831	3.782	1.510	4.076

NO ACCOUNT IS TAKEN OF GROUND CONTACT RESISTANCE.

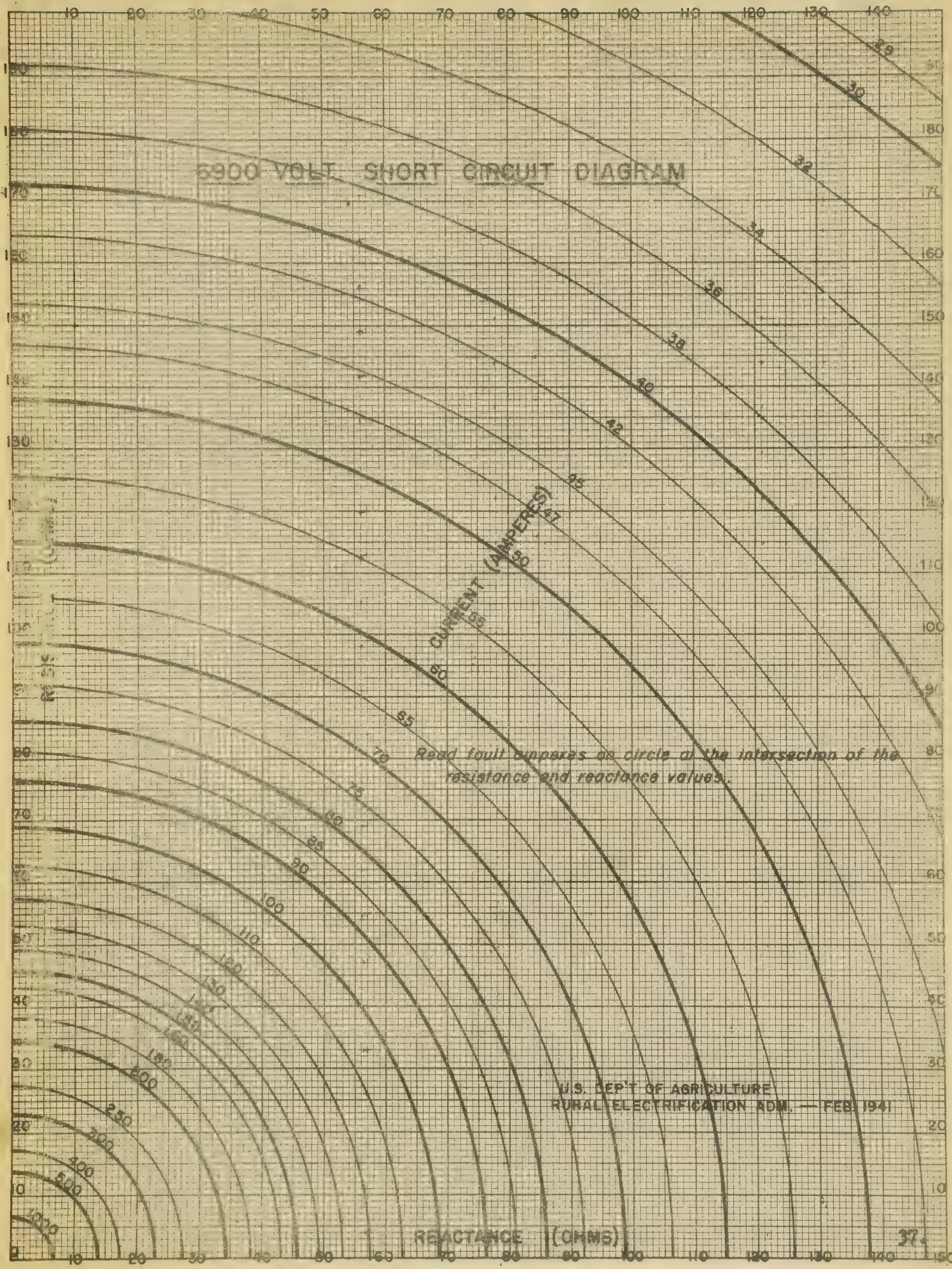
6900 VOLT SHORT CIRCUIT DIAGRAM
CURRENT (AMPERES)
Read fault amperes on circle at the intersection of the resistance and reactance values.
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM. — FEB. 1941
REACTANCE (OHMS)
RESISTANCE (OHMS)

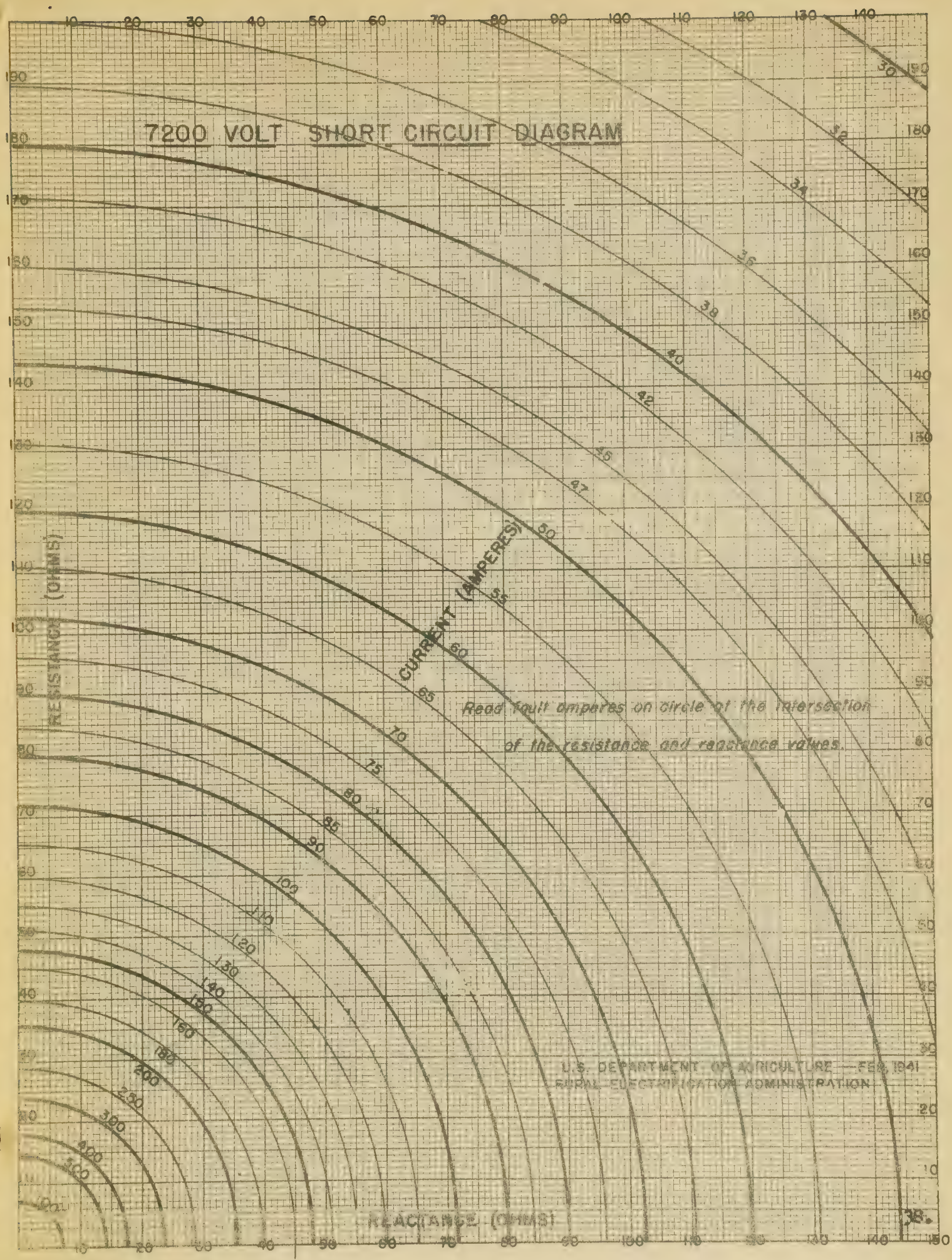
7200 VOLT SHORT CIRCUIT DIAGRAM
CURRENT (AMPERES)
RESISTANCE (OHMS)
REACTANCE (OHMS)
Read fault amperes on circle of the intersection of the resistance and reactance values.
U.S. DEPARTMENT OF AGRICULTURE — FEB. 1941
RURAL ELECTRIFICATION ADMINISTRATION
38.

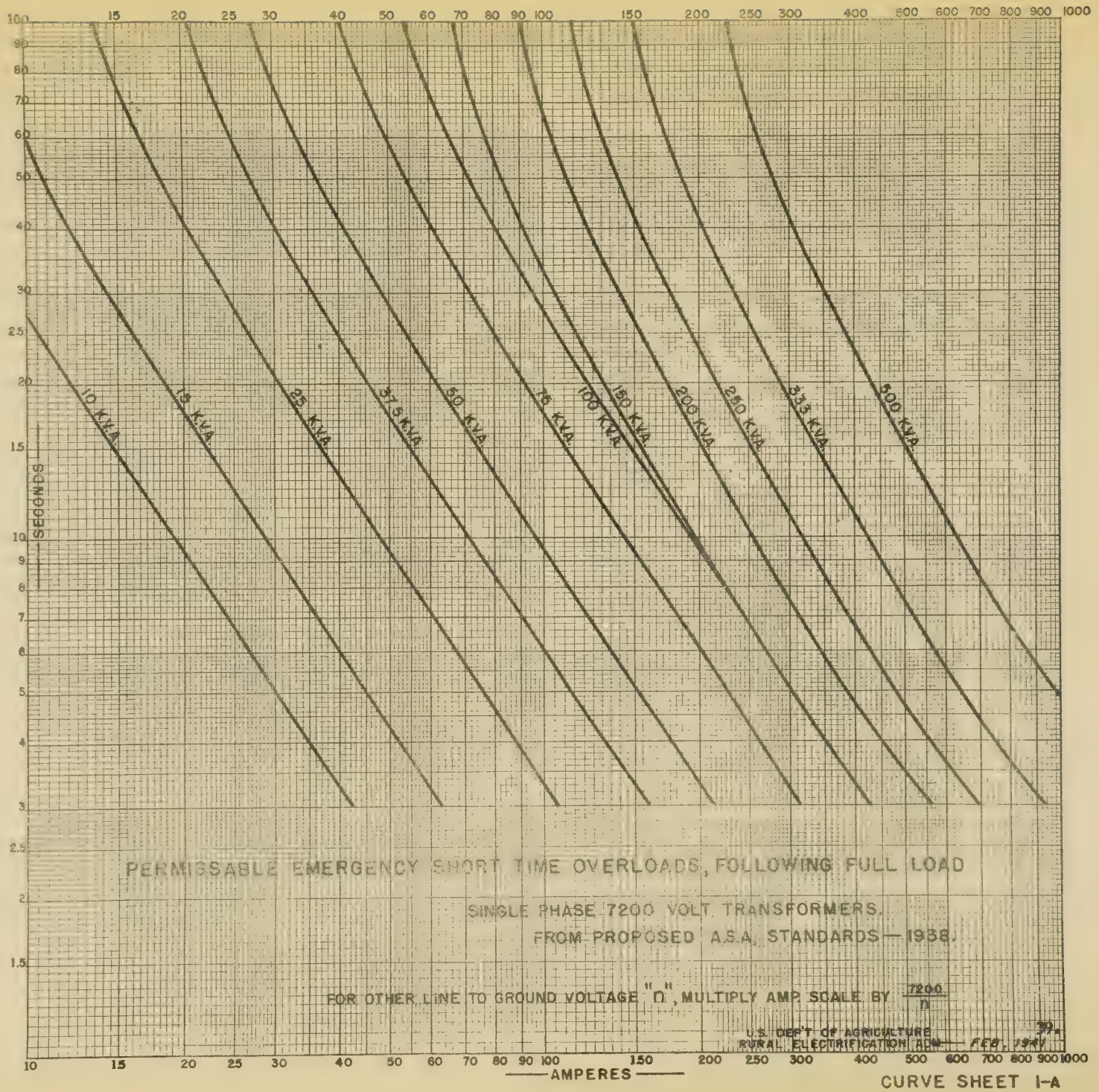

CURVE SHEET I-A

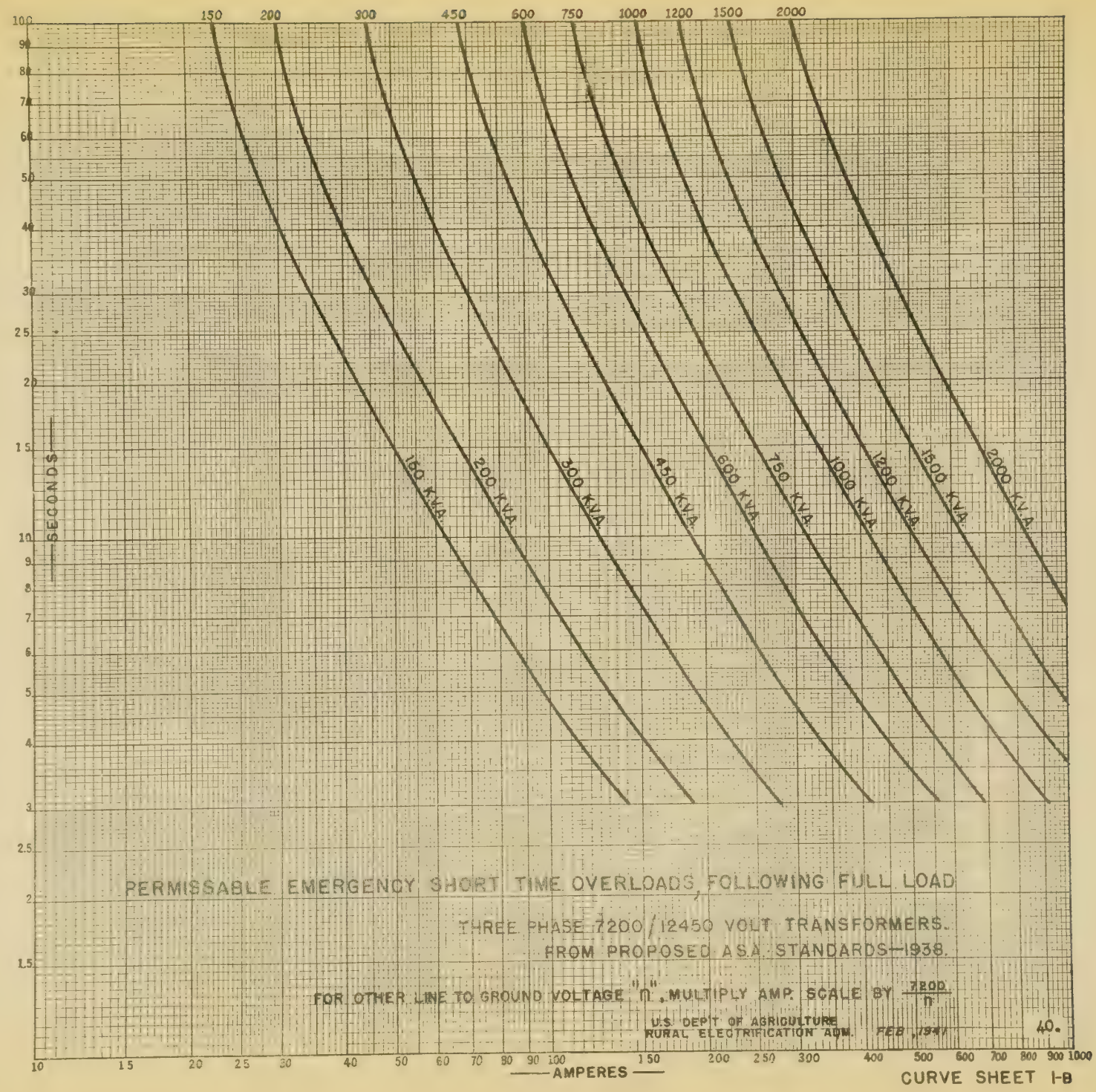

CURVE SHEET I-B

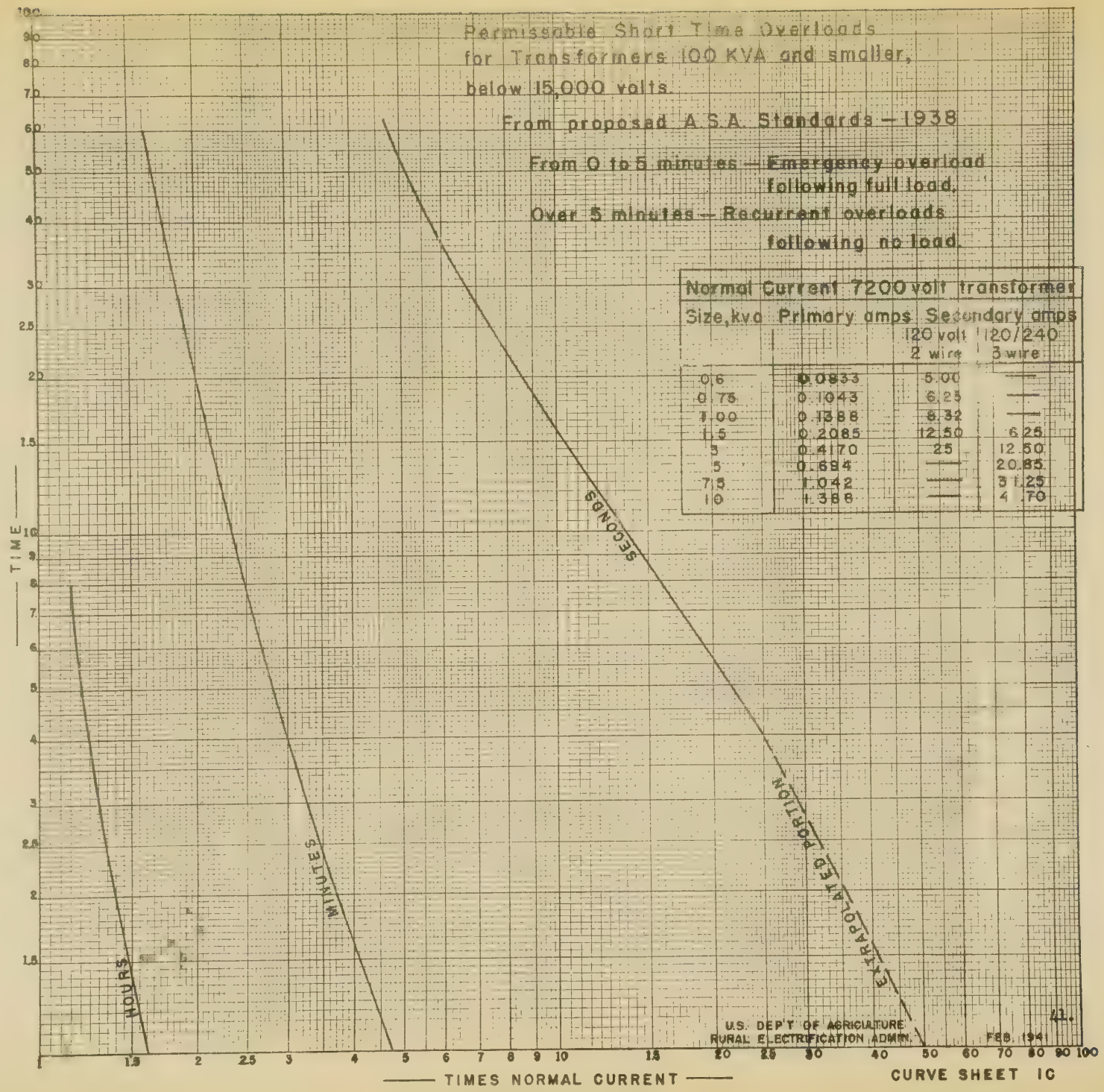

Normal Current 7200 volt transformer			
Size, kva	Primary amps	Secondary amps 120 volt 2 wire	Secondary amps 120/240 3 wire
0.6	0.0833	5.00	—
0.75	0.1043	6.25	—
1.00	0.1388	8.32	—
1.5	0.2085	12.50	6.25
3	0.4170	25	12.50
5	0.694	—	20.85
7.5	1.042	—	31.25
10	1.388	—	41.70

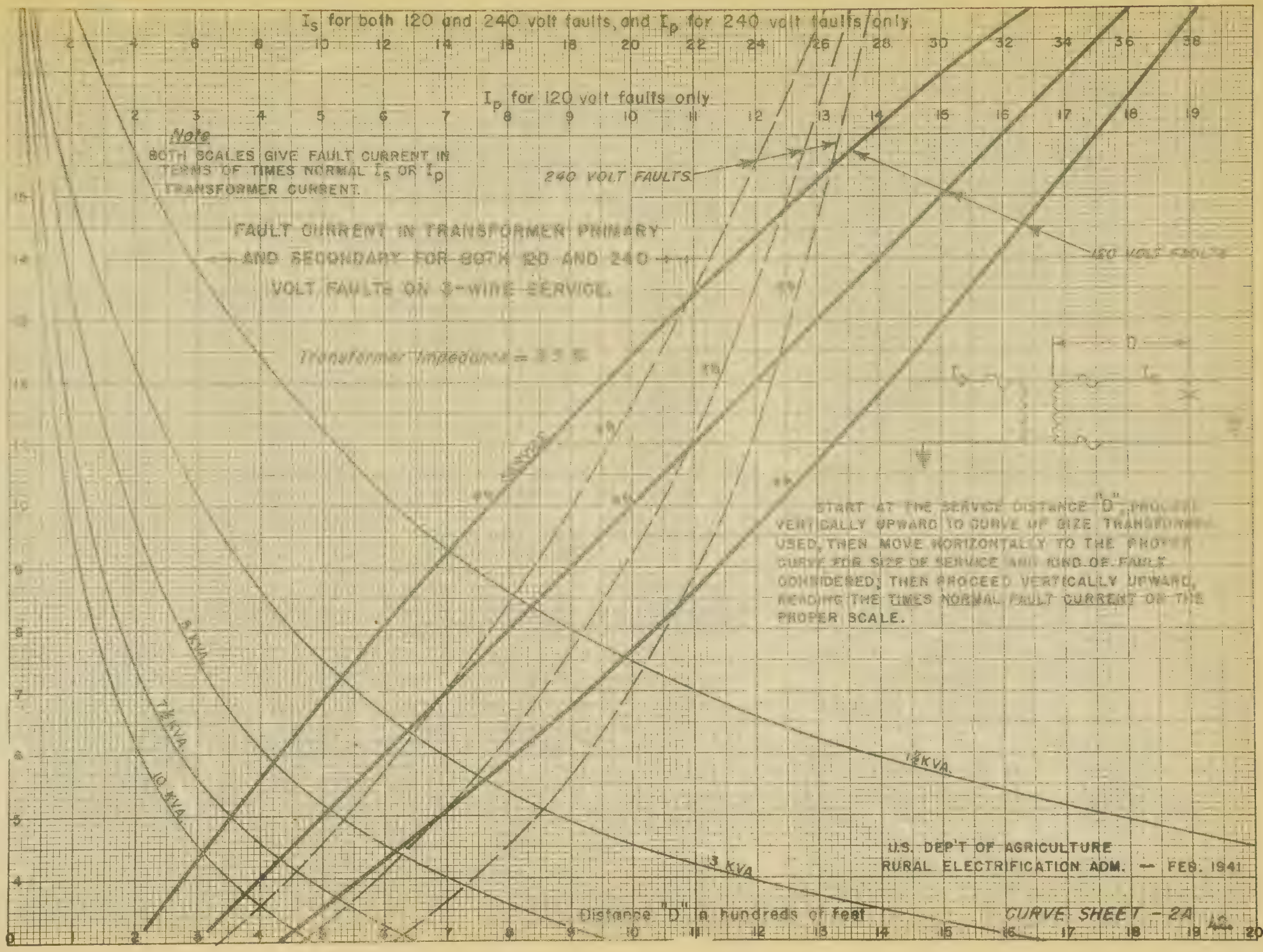
I_s for both 120 and 240 volt faults, and I_p for 240 volt faults only.
I_p for 120 volt faults only
Note
BOTH SCALES GIVE FAULT CURRENT IN TERMS OF TIMES NORMAL I_s OR I_p TRANSFORMER CURRENT.
240 VOLT FAULTS
120 VOLT FAULTS
FAULT CURRENT IN TRANSFORMER PRIMARY AND SECONDARY FOR BOTH 120 AND 240 VOLT FAULTS ON 3-WIRE SERVICE.
Transformer Impedance = 3.5 %
D
START AT THE SERVICE DISTANCE "D", PROCEED VERTICALLY UPWARD TO CURVE OF SIZE TRANSFORMER USED, THEN MOVE HORIZONTALLY TO THE PROPER CURVE FOR SIZE OF SERVICE AND KIND OF FAULT CONSIDERED; THEN PROCEED VERTICALLY UPWARD, READING THE TIMES NORMAL FAULT CURRENT ON THE PROPER SCALE.
15 KVA
10 KVA
7½ KVA
5 KVA
3 KVA
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM. — FEB. 1941
Distance "D" in hundreds of feet
CURVE SHEET - 2A

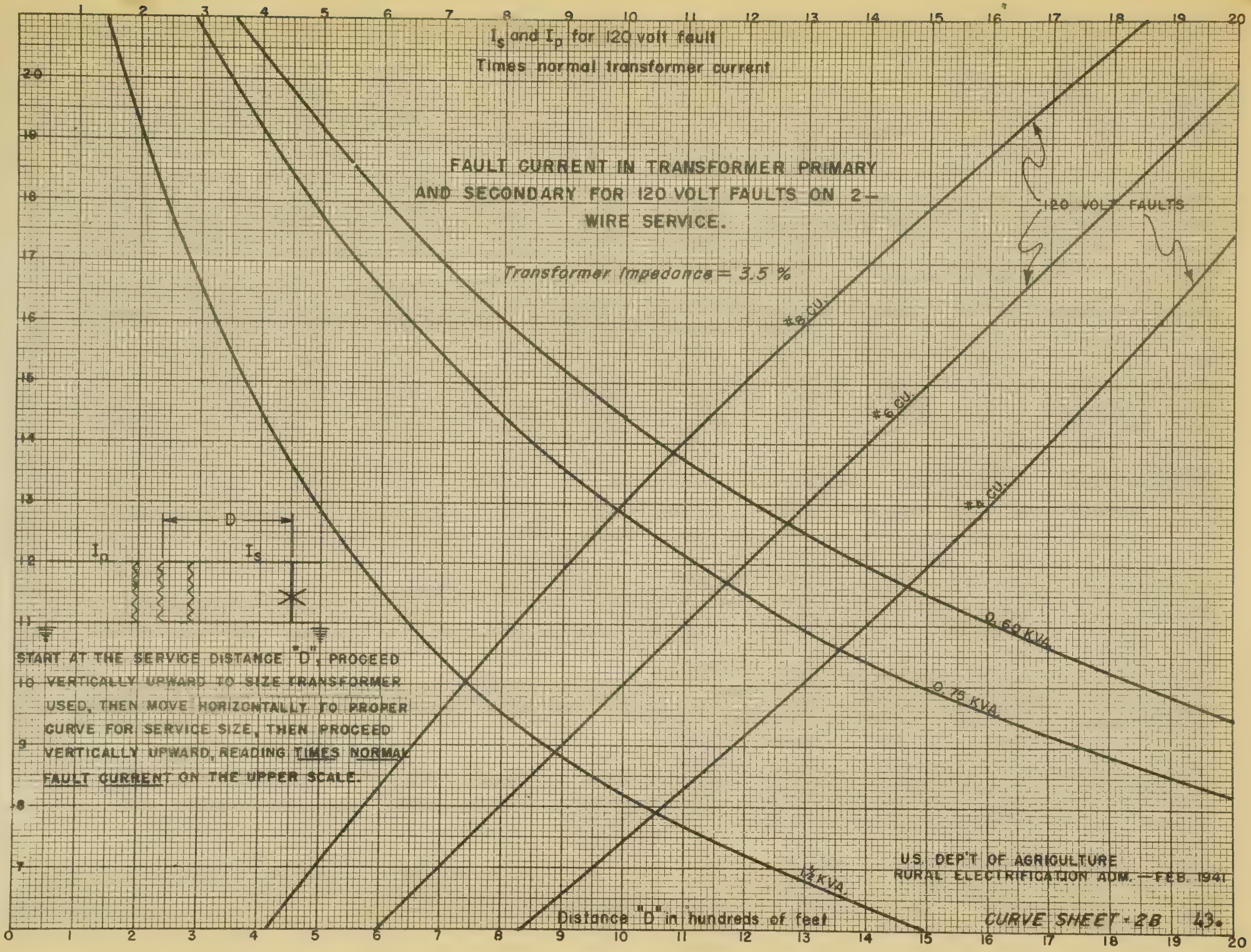
I_s and I_p for 120 volt fault
Times normal transformer current
FAULT CURRENT IN TRANSFORMER PRIMARY AND SECONDARY FOR 120 VOLT FAULTS ON 2-WIRE SERVICE.
Transformer Impedance = 3.5 %
120 VOLT FAULTS
#8 CU.
#6 CU.
#4 CU.
0.50 KVA.
0.75 KVA.
1½ KVA.
D
I_p
I_s
START AT THE SERVICE DISTANCE "D", PROCEED TO VERTICALLY UPWARD TO SIZE TRANSFORMER USED, THEN MOVE HORIZONTALLY TO PROPER CURVE FOR SERVICE SIZE, THEN PROCEED VERTICALLY UPWARD, READING TIMES NORMAL FAULT CURRENT ON THE UPPER SCALE.
Distance "D" in hundreds of feet
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM. — FEB. 1941
CURVE SHEET - 2B

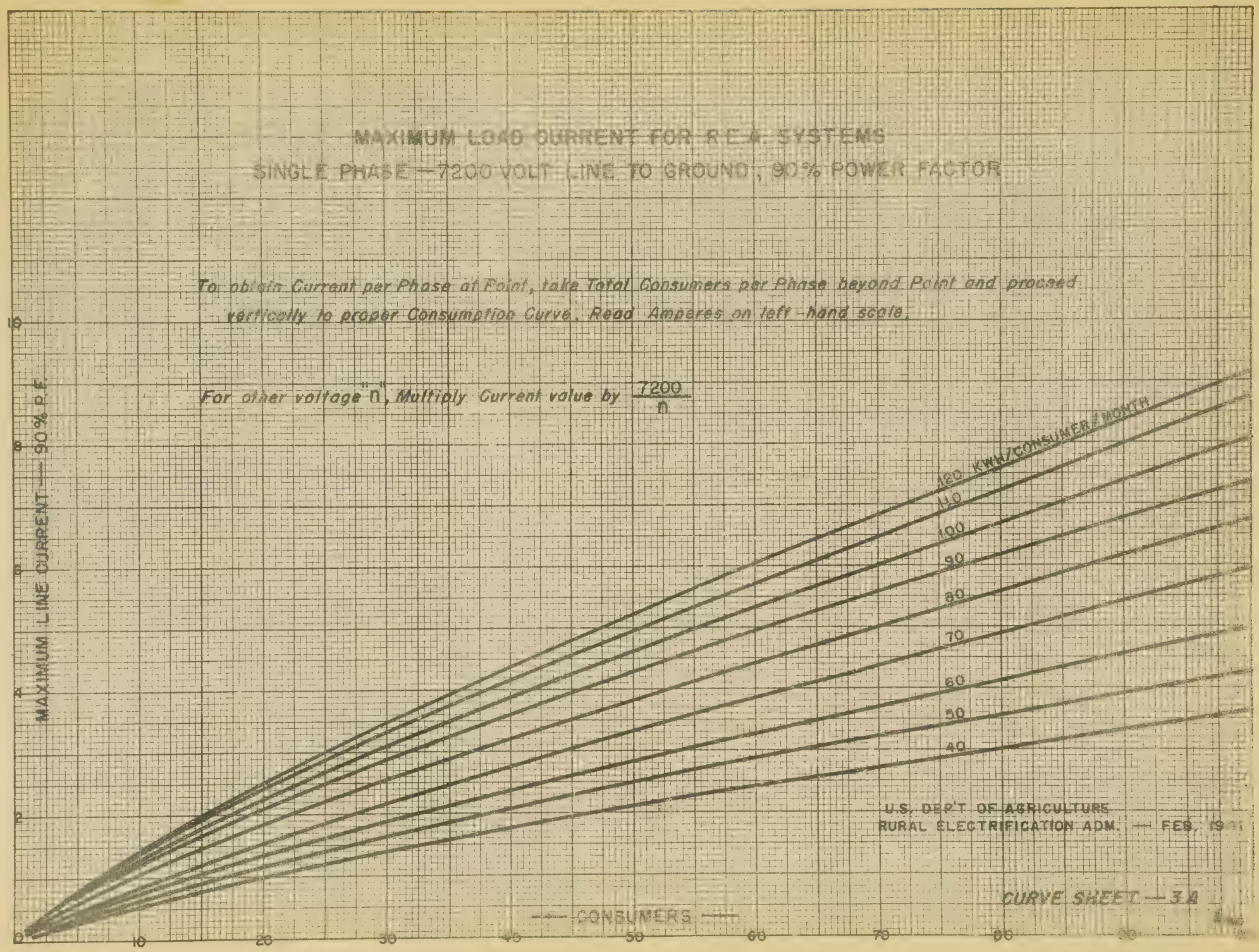
MAXIMUM LOAD CURRENT FOR R.E.A. SYSTEMS
SINGLE PHASE — 7200 VOLT LINE TO GROUND, 90% POWER FACTOR
To obtain Current per Phase at Point, take Total Consumers per Phase beyond Point and proceed vertically to proper Consumption Curve. Read Amperes on left-hand scale.
For other voltage "n", Multiply Current value by 7200/n
MAXIMUM LINE CURRENT — 90% P.F.
120 KWH/CONSUMER/MONTH
110
100
90
80
70
60
50
40
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM. — FEB. 19
CURVE SHEET — 3A
CONSUMERS
0
10
20
30
40
50
60
70
80
90
2
4
6
8
10

MAXIMUM LOAD CURRENT FOR R.E.A. SYSTEMS

SINGLE PHASE – 7200 VOLT LINE TO GROUND, 90% POWER FACTOR

To obtain Current per Phase at Point, take Total Consumers per Phase beyond Point and proceed vertically to proper Consumption Curve. Read Amperes on left-hand scale.

For other voltage "n", Multiply Current value by $\frac{7200}{n}$

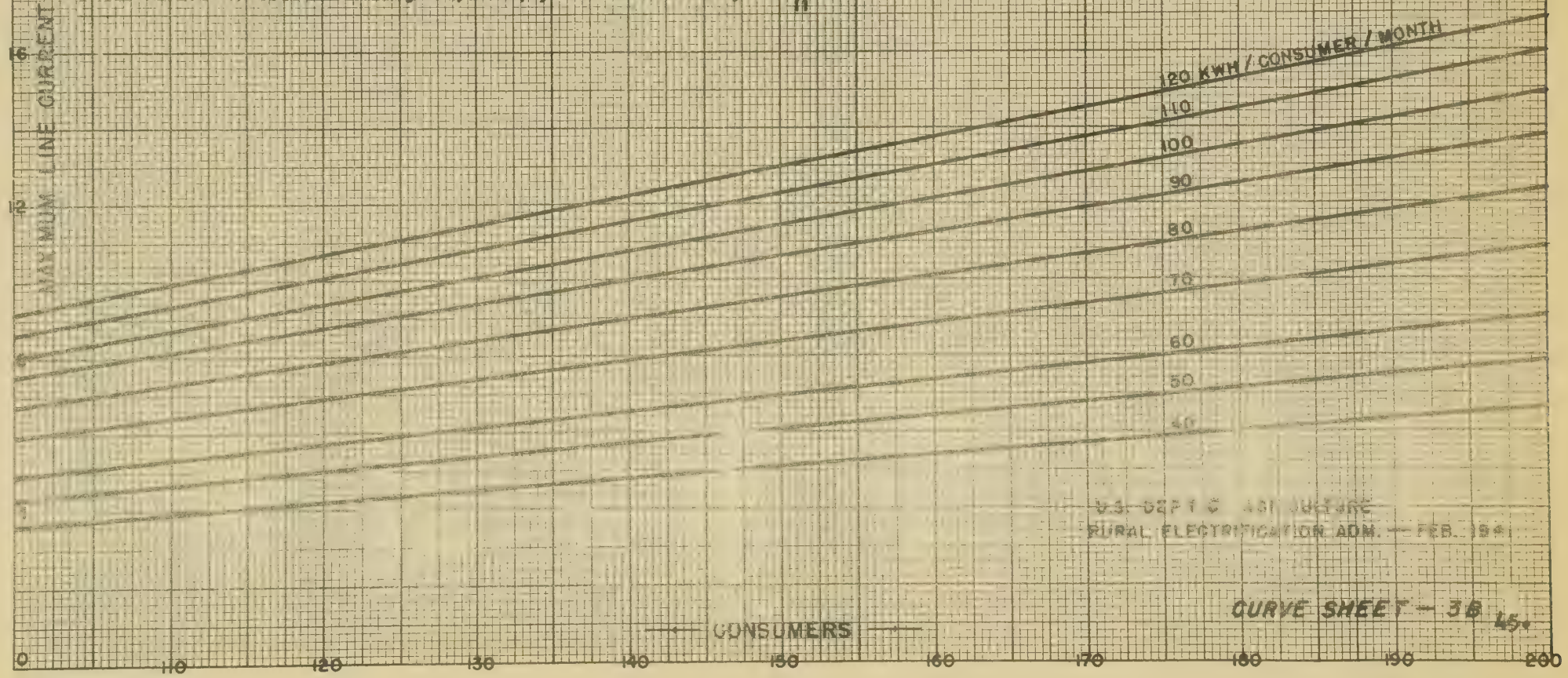

U.S. DEPT. OF AGRICULTURE
RURAL ELECTRIFICATION ADM. — FEB. 194

CURVE SHEET – 3Ø 45.

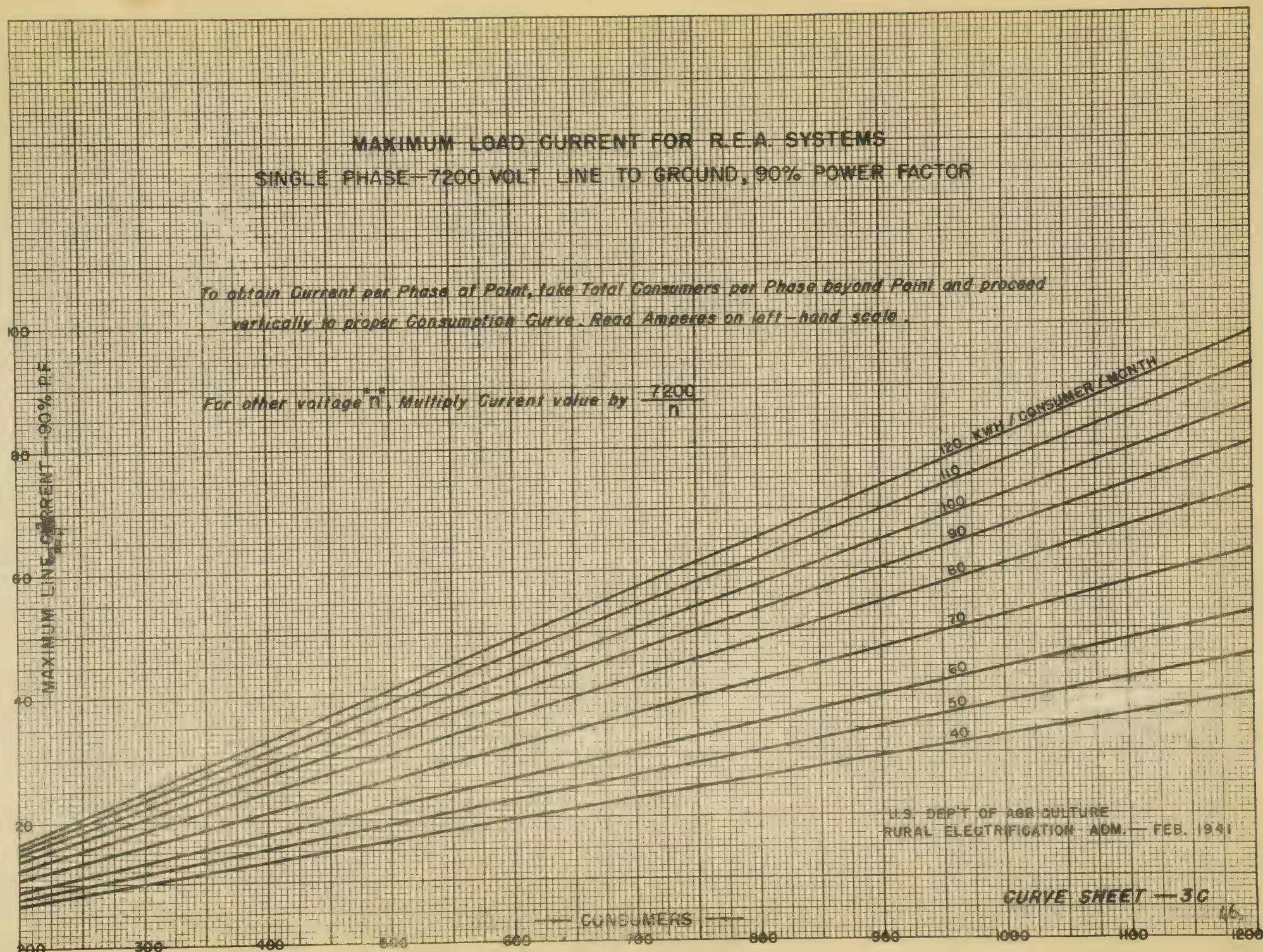
MAXIMUM LOAD CURRENT FOR R.E.A. SYSTEMS
SINGLE PHASE—7200 VOLT LINE TO GROUND, 90% POWER FACTOR
To obtain Current per Phase at Point, take Total Consumers per Phase beyond Point and proceed vertically to proper Consumption Curve. Read Amperes on left-hand scale.
For other voltage "n", Multiply Current value by 7200/n
MAXIMUM LINE CURRENT — 90% P.F.
120 KWH / CONSUMER / MONTH
110
100
90
80
70
60
50
40
100
80
60
40
20
200
300
400
500
600
700
800
900
1000
1100
1200
CONSUMERS
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM. — FEB. 1941
CURVE SHEET — 3C

FORM TS-2

U.S. DEP'T OF AGRICULTURE RURAL ELECTRIFICATION ADMINISTRATION	SECTIONALIZING STUDY	Sheet ____ of ____ sheets PROJECT ----------
	SUBMITTED BY ----------	DATE ----------
	CHECKED BY ----------	DATE ----------

TYPE OF FAULT CALCULATED
(Indicate by check (✓) in box provided below)

THREE PHASE ☐ LINE TO LINE ☐ LINE TO GROUND ☐

A — IMPEDANCE OF SOURCE

ohms

1. PLANT

(a) DIRECT AXIS TRANSIENT REACTANCE — FULL LOAD ---------
(b) NEGATIVE SEQUENCE " — " " ---------
(c) DIRECT AXIS TRANSIENT REACTANCE — MINIMUM " ---------
(d) NEGATIVE SEQUENCE " — " " ---------
(e) (a) + (b), EQUIVALENT REACTANCE ON LOAD SIDE ---------
(f) (c) + (d), " " " " " ---------

2. TIE LINE

(g) RESISTANCE REFERRED TO LOAD VOLTAGE ----------
(h) REACTANCE " " " " ----------

3. TOTAL

(i) MAXIMUM LOAD
1. RESISTANCE EQUALS (g) ----------
2. REACTANCE " (e) + (h) ----------

(j) MINIMUM LOAD
1. RESISTANCE " (g) ----------
2. REACTANCE " (f) + (h) ----------

4. FOR LARGE SUPPLY SYSTEM ONLY

(k) MAXIMUM LOAD REACTANCE ----------
(l) MINIMUM " " ----------

B — IMPEDANCE OF SUBSTATION

(m) Z_T ----------
(n) R_T ----------
(o) X_T ----------

C — TOTAL IMPEDANCE OF SOURCE AND SUBSTATION

(p) MAXIMUM CONDITIONS
1. $R = (n) + (i_1)$ ----------
2. $X = (o) + (i_2)$ or (k) ----------

(q) MINIMUM CONDITIONS
1. $R = (n) + (j_1)$ ----------
2. $X = (o) + (j_2)$ or (l) ----------

FORM TS-3

U.S. DEPARTMENT OF AGRICULTURE
RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY

SHEET _____ OF _____ SHEETS

PROJECT _____

SUBMITTED BY _____, DATE _____ CHECKED BY _____, DATE _____

r	s	t	u	v	w	x	y	z	aa	ab	ac	ad	ae	af	ag	ah
POINT	PRECEDING POINT ON LINE TOWARD SUBSTATION	MILES FROM PREVIOUS POINT ON LINE TOWARD SUBSTATION	COPPER CONDUCTIVITY SIZE, SECTION FROM PREVIOUS POINT	TYPE OF FAULT CALCULATED	RESISTANCE "R", SECTION FROM PREVIOUS POINT	RESISTANCE "R", BACK TO SUBSTATION	FOR MAX. CONDITION, TOTAL RESISTANCE TO SOURCE = $x + p_1$	FOR MIN. CONDITION, TOTAL RESIST TO SOURCE = y + FAULT RESIST.	REACTANCE "X", SECTION FROM PREVIOUS POINT	REACTANCE "X", BACK TO SUBSTATION	FOR MAX. CONDITION, TOTAL REACTANCE TO SOURCE = $ab + p_2$	FOR MIN. CONDITION, TOTAL REACTANCE TO SOURCE = $ab + q_2$	FOR MAX. CONDITION, TOTAL IMPEDANCE TO SOURCE = $\sqrt{y^2 + ac^2}$	FOR MIN. CONDITION, TOTAL IMPEDANCE TO SOURCE = $\sqrt{z^2 + ad^2}$	MAX. CURRENT "I" = $\frac{\text{VOLTAGE}}{ae}$	MIN. CURRENT "I" = $\frac{\text{VOLTAGE}}{af}$

FORM TS-4

U.S. DEP'T OF AGRICULTURE RURAL ELECTRIFICATION ADMINISTRATION	SECTIONALIZING STUDY	Sheet _____ of _____ sheets PROJECT
	SUBMITTED BY _____, DATE _____ CHECKED BY _____, DATE _____	

This Study is based on the use of the following makes of Sectionalizing Equipment:—

	BREAKERS	FUSE LINKS
1. Substation — Supply Side		PRESTO — TYPE "K"
2. Substation — Load Side	OC — TYPE LM.	SUPER XX — 10
3. Lines	" " "	" "

POINT	PRESENT DEVICE		DEVICE TO BE INSTALLED		REMARKS
	TYPE	DISPOSITION	TYPE	RATING	

Sample Problem

This is a sample only. It does not necessarily indicate an actual case, and the results are not necessarily those recommended by REA. The sample only illustrates a procedure. Attached is scale map A, page 56, of Somestate 39 Smith, showing tentative sectionalizing. The project receives power from a Diesel plant at point A. This plant has four 4800-volt units of 1000 kva each, three of which run during peak load, and one of which runs at light load. The constants of all generators are as follows:

(1) Direct-axis transient reactance - 0.315 per unit (31.5 percent)

(2) Negative sequence reactance - 0.195 per unit (19.5 percent)

The plant is considered sufficiently large so that decrement may be neglected. The three-mile line AB is #4/0 copper with 4-foot equivalent spacing, and the voltage is 4800, line-to-line. The REA substation has three 200 kva transformers of 3.95% impedance each connected delta-wye, with 7200 volts line-to-ground on the load side. Tentative positions for sectionalizing devices have been selected as shown on the key map A, and devices have been tentatively selected as shown. The maximum fuse at B allowed by the power supply company is a 200-ampere Presto type K power fuse, with melting time curve as shown by plate "A", page 59. Plate "B", page 60, shows part of the total clearing time curves for all sizes of the Super #XX-1D fuse link, plate "C", page 61, the remaining part of these total clearing time curves and the first opening time of the OC-type LM oil circuit recloser, and plate "D", page 62, the equivalent heating effect of the recloser to lockout. There is an oil circuit breaker in the plant controlled by an Electro type PB relay, which is connected to the main circuit with a 200/5 current transformer.

Table (1), pages 57 & 58, is a coordination table for the Super fuse link. Two, three and five kva distribution transformers are fused with a 2-ampere Super #XX-1D fuse. There is no larger size of transformer than 5 kva on the project. The peak load may be taken as 1 kva per phase-mile throughout. Make a complete sectionalizing study of the project.

Sample Problem - Solution

Forms TS-2____ and TS-3____ are self-explanatory. A fault resistance of 30 ohms was used in obtaining the minimum fault current for a line-to-ground fault. The maximum and minimum fault currents after calculation are placed directly on the key map as shown. The line-to-line and three phase faults were calculated at the substation and at points H and R. The minimum fault current for the section controlled by fuse D is at points H and E (second sectionalizing point from substation) and is 91.9 amperes. From curve sheet 1A, the time in which the 200 kva transformers would be damaged at 91.9 amperes is 92 seconds. From Plate "B", the total clearing time of a 45-ampere Super #XX-1D fuse is 6.4 seconds at 91.9 amperes.

Since D is a 3-shot, 3 times 6.4 is a total clearing time of 19.2 seconds, which is considerably below the failure time of the transformer, and hence 3-shot, 45-ampere fuses at D are safe.

The total clearing time of a 50 ampere fuse at 91.9 amperes is 60 seconds, and of three of these is 180 seconds, and hence the 50 ampere fuses would not be safe. If desired, the 3-shot at D could be fused as a 10-45-45 combination. The use of the 10-ampere fuse in the first shot can be expected to lessen the number of trips to outlying fuses, and lower the outage time. Since the load is only about 40 kva, or about 6 amperes, the 10-ampere fuse will carry the normal maximum load.

The maximum fault current at D is 253 amperes, a line-to-ground value. From formula (13) this gives 380 amperes through fuse B, with position D fused 10-45-45, the total clearing time for D at 253 amperes is 0.029 + 0.305 + 0.305 = 0.639 seconds, from Plate "C", (neglecting reclosing time). Since Plate "A" shows melting time of the primary fuse at B, divide 0.639 by 0.75 to obtain 0.852 seconds as the value to use to prevent damage of fuse B. 0.852 seconds on Plate "A" gives the current in percent of the fuse rating at 360%. Since the supply current is 380 amperes, the fuse size must be $\frac{380}{3.60} = 105.6$ amperes. From the catalog, the next larger sizes are 150 and 200 amperes.

To check coordination for three-phase faults, we see that the maximum three phase fault at D is 177 amperes, which is 460 amperes through fuse B by formula (14). Total clearing time for the fuses at D at 177 amperes is 0.048 + 0.64 + 0.64 = 1.33 seconds, and this divided by 0.75 gives 1.77 seconds damage time, which gives the current in percent of fuse B rating as 255% on plate "A". This fuse size is therefore $\frac{460}{2.55} = 180.5$ amperes.

The standard 200 ampere size will therefore provide coordination for three phase faults.

The maximum line-to-line fault current is 166 amps, or 498 amperes on the low voltage side by formula (15). The total clearing time of fuses at D at 166 amperes is 1.55 seconds. Repeating the above process, fuse B must be $\frac{498}{2.40} = 208$ amperes in size.

This is somewhat over the 200 limiting figure, but rather than reduce the load side fuse sizes, operation will be continued on this basis, taking a chance on an occasional supply side fuse failure. (Since three phase and line-to-line faults are rare compared to line-to-ground faults, it may often be necessary to coordinate using the line-to-ground formula.) It can be seen that the line-to-line faults are the worst condition for supply and load side coordination.

To select the breaker at C, the procedure is as follows: the second sectionalizing point on the other main branch is R, where the minimum fault current is 83.8 amperes. From Plate "C", the 50 ampere recloser initially opens at a minimum of 130 amperes, and hence cannot be used at point C because there is insufficient pick-up current. The 35 ampere recloser opens at a minimum of 74 amperes, which is less than 83.8 amperes and hence may be used. The first opening time of the 35 ampere breaker on 83.8 amperes is 0.47 seconds, and this times 3 is 1.41 seconds, which is much lower than the damaging time of the 200 kva substation transformer on this current, and hence the breaker is safe in protecting the substation transformers. If desired, a fuse could be used between breaker C and the substation to give back-up protection for currents less than 74 amperes.

To check coordination of the breaker at C with fuse B, use the equivalent heating to lock-out curves, Plate "D". At 166 amperes, this time is 0.105 seconds. The line-to-line fault current referred to the supply side is 498 amperes (see above), or 249% of the 200 ampere fuse rating previously selected. At the 249% point on Plate "A", we find the time to melt fuse B is 1.85 seconds, or to damage it is about 0.75(1.85) = 1.39 seconds. The damage time of 1.39 seconds is over ten times the 0.105 seconds heating to lock-out time of the breaker and hence coordination is satisfactory. (For a breaker, further check must sometimes be made at the minimum fault current, but here the time spread is so great this is not necessary).

The sectionalizing apparatus at the substation is therefore definitely selected as follows:

(1) Fuse B - 200 ampere Presto Type K
(2) Position D - 10-45-45 ampere fuses, Super #XX-1D
(3) Position C - 35 ampere recloser OC, Type LM

Now start at point M using the fuse coordination table. The maximum line-to-ground fault current at point M is 138 amperes. A 2 ampere transformer fuse (protecting link--see left-hand column) will protect a 15 ampere fuse (protected link--see top row) up to 140 amperes. Hence tentatively use a 15 ampere fuse at points L and M. From Plate "B", the current necessary to blow the 15 ampere fuse in 100 seconds is 21 amperes, and since the minimum fault current at the end of the long line (N) is 72 amperes, the 15 ampere fuse is satisfactory from this standpoint.

At point K, a 20 ampere fuse is necessary to be protected by a 3 ampere transformer fuse, and the same is true at points I, J and F. The maximum fault current at I and F is 180.5 amperes, and these cutouts are 2-shots. The table shows that a 20 ampere 2-shot (left-hand column) will protect a 40 ampere fuse up to 200 amperes; however, a 40 ampere fuse at points E or H will not coordinate with the previously chosen 45 ampere fuse at D. If we make the cutouts at I and F single-shots, 30 ampere fuses can be used at E and H, since a 30 ampere fuse will be protected by a single 20 ampere fuse up to 200 amperes fault current. The 30 ampere fuses at E and H will now coordinate with the 45 ampere links at D, providing E and H are two-shot cutouts, but not if the cutout at H is a three-shot.

An alternate solution might be to fuse points F, I, J, K, L, and M with 10 ampere links. Then 2-shot 10 ampere fuses at F and I would protect 30 ampere fuses at E and H. In the latter case, the fuses at points F, I, J, K, L, and M would not coordinate properly with the transformer cutout fuses, but extra shots could be added at all sectionalizing points, so that primary outages could be reduced. In fact, 2-shot cutouts could also be installed at points J, K, L and M, if desired.

This is the solution shown in the final sample map. (It is not necessarily to be preferred. Local judgment must rule in cases of this kind). In the final set-up shown, failure of a transformer fuse on any of the branch lines controlled by 10 ampere line fuses would also probably damage the first shot in the line fuse. Hence the lineman should replace the first line sectionalizing fuse link upon such an occurrence. Also, the use of the 10-ampere fuse in the first shot at the substation will provide three-shot protection for all main lines and save lengthy service trips, but will of course not coordinate properly with the branch line 10-ampere fuse links. Hence, a fault on the branch line may damage or blow the first fuse link at D at the same time as the branch fuse blows. It can be seen that in any case a 3-shot 30-ampere cutout at H will not coordinate with the 45-ampere fuse at D, and hence a two-shot must be used.

Turning to the other main branch, it can be seen that if a 35 ampere reclosing breaker is installed at C, a 25 ampere size can be installed at R and 12 ampere sizes at S and V. (Since there are gapped transformers beyond S, there <u>must</u> be a recloser at point S). The minimum current in the section controlled by the breaker R is 69.9 amperes, which is in excess of the 62-ampere "pick-up" point. The minimum in the section controlled by breaker V is 55 amperes, which is in excess of the 30 ampere "pick-up" point for the 12 ampere breaker. Similarly, reclosing breaker S is satisfactory.

From Plate "C", the largest fuse size which will coordinate with a 12 ampere breaker at V is a 3 ampere size. In other words, with any fuse larger than a 3 ampere size, the breaker will open on a fault before the fuse. Also, it can be seen from the table that a 3 ampere fuse will not be protected by a 2 ampere transformer fuse for any value of fault current. There are three possible solutions to this problem.

(1) Do not use any fuses at Y, Z, AA, AB, or AF, but use manual switches at these points.
(2) Use a fuse at V instead of a breaker.
(3) Fuse cutouts at points Y, Z, AA, AB, and AF, or some of them, with 2- or 3-shot 3 ampere fuses.
(4) Fuse cutouts at points Y, Z, AA and AB with 10 ampere single-shot fuses.

If (1) is followed, manually operated switches could be placed at these points. If (2) is followed, the first shot of the line fuses will blow almost every time a transformer fuse blows, but since there will be one or two remaining shots, the line will remain in service. In this case, the lineman must examine the line fuses and replace the first shot after each such occurrence. In case (4) is used, it can be seen that the breaker will

trip on any fault in the section beyond the breaker. Temporary surges will be automatically removed, as the breaker will reclose. If the fault is permanent, the breaker will lock out. The lineman can then short out the breaker with a 20 ampere fuse. The particular branch fuse will then blow, the breaker can be reclosed, and the faulty line will be isolated.

Let us assume local conditions favor solution (3). Two-shot or three-shot 3 ampere fuses will then be installed at Y, Z, AA, and AB. It would obviously be useless to install a fuse at AF, since there could be no coordination between AF and AA. (Many operators favor solution (4)).

From the coordination table, fuse X should be a 15 ampere fuse, and fuse U a 25 ampere fuse, for proper coordination with a 2 ampere distribution transformer cutout; however, recloser R is a 25 ampere size, and from Plate "C" the largest fuse which can coordinate with this is a 10 ampere size. Hence U and T must be made two- or three-shot with 10 ampere fuses.

The fuse at X can then be eliminated or replaced with a manual switch to provide for manual sectionalizing in case of trouble. The same applies to W, except that two-shot 2 ampere fuses could be placed at W, if desired.

The minimum current at AC is 60.7 amperes, which is sufficient to blow a 10 ampere fuse at T.

(12 ampere reclosers could also be placed at U and T, if the investment were considered justified.)

The recloser at S has already been selected as 12 ampere.

Fuse Q must be a 20 ampere size, and points P and O must have 20 ampere fuses for proper coordination with the distribution transformer cutouts. These points may be made one-, two-, or three-shot, according to the investment justified.

From Plate "C", 20 ampere fuses at O and P under a 194 ampere maximum fault will coordinate satisfactorily with the 35 ampere breaker at C. For 107 amperes, coordination is still satisfactory. For values between, however, the coordination is very close. If the fuse links are of the spring-type, or the cutout mechanically increases the gap between the link, coordination will probably be satisfactory.

Table (2)

Characteristics of Electro Type PB Relay

		Time in Seconds to Trip									
	1.5	1.3	2.1	4.0	5.3	6.6	7.9	9.3	10.8	12.0	13.3
	2	0.9	1.7	2.5	3.4	4.2	5.0	5.9	6.7	7.5	8.4
Times	3	0.7	1.2	1.7	2.3	2.8	3.4	3.9	4.5	5.0	5.5
Current	5	0.5	0.9	1.2	1.7	2.0	2.4	2.8	3.2	3.6	4.0
Tap	10	0.4	0.7	0.9	1.2	1.5	1.8	2.1	2.3	2.6	2.9
Setting	20	0.3	0.5	0.7	0.9	1.1	1.3	1.5	1.8	2.0	2.2
	30	0.2	0.4	0.6	0.8	1.0	1.2	1.3	1.5	1.7	1.9
	50	0.2	0.3	0.5	0.7	0.8	1.0	1.1	1.3	1.5	1.6
Time Lever Setting		1	2	3	4	5	6	7	8	9	10

Taps are 4, 5, 6, 7, 10, 12 and 15 amperes.

Table (2) indicates the characteristics of the breaker relay in the plant. Since the current transformer is 200/5 ratio, one ampere on the relay is equal to 40 amperes in the main circuit. The maximum line-to-ground fault current referred to the supply side is 380 amperes, which melts the high side fuse in about 3.9 seconds. The clearing time is around 4 seconds. Therefore, the relay time must be more than 4 seconds for 9.5 amperes. If we use a 6 ampere tap, this would be 1.58 times normal, and, from Table 2, a time lever setting of 4 or over will provide coordination. The minimum line-to-ground fault current is 187 amperes, referred to the supply side, which is less than the fuse rating. The relay must therefore be set to "pick up" at a value in excess of the continuous capacity of the fuse. Referring to the melting time curve, Plate "A", the relay must pick up at a greater current than $\frac{280}{40} = 7$ amperes. We must therefore use the 7 ampere relay tap or greater.

Now, by plotting characteristic curves, Plate "F", page 64, it can be seen that the relay must take about four seconds to operate on about 162 amperes (referred to 7200 volt side by formula (13), or 10.5 relay amperes (1.5 times normal). Time lever setting 3 seems to satisfy these requirements, so we plot the entire curve for tap setting 7 and time lever setting 3, and find that proper coordination occurs over the entire range.

Whether conversion formula (13), (14), or (15) is used makes no difference insofar as the relationship between supply side characteristics is concerned. Line-to-line faults (formula (15)) are generally the criterion faults insofar as coordination of the load and supply side devices are concerned. Plate F shows coordination for three phase faults, and plate G, page 65, for line-to-ground faults. A line-to-line chart could similarly be made.

The final map B, page 73, prepared as shown, giving selected devices and sizes, should be left for the guidance of the project operating personnel. It should be noticed that the fault current values are left on the final map. These are indicated so that when future additions to the project are made, the entire set of values will not have to be recalculated.

(This example does not necessarily represent the most complete installation. For example, additional short-branch lines might be fused. The example is only for the purpose of method explanation.)

DEPARTMENT OF AGRICULTURE

RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY "KEY MAP" A

PROJECT

SOMESTATE-39-SMITH

SUBMITTED BY John Doe DATE Feb. 1941 CHECKED BY DATE

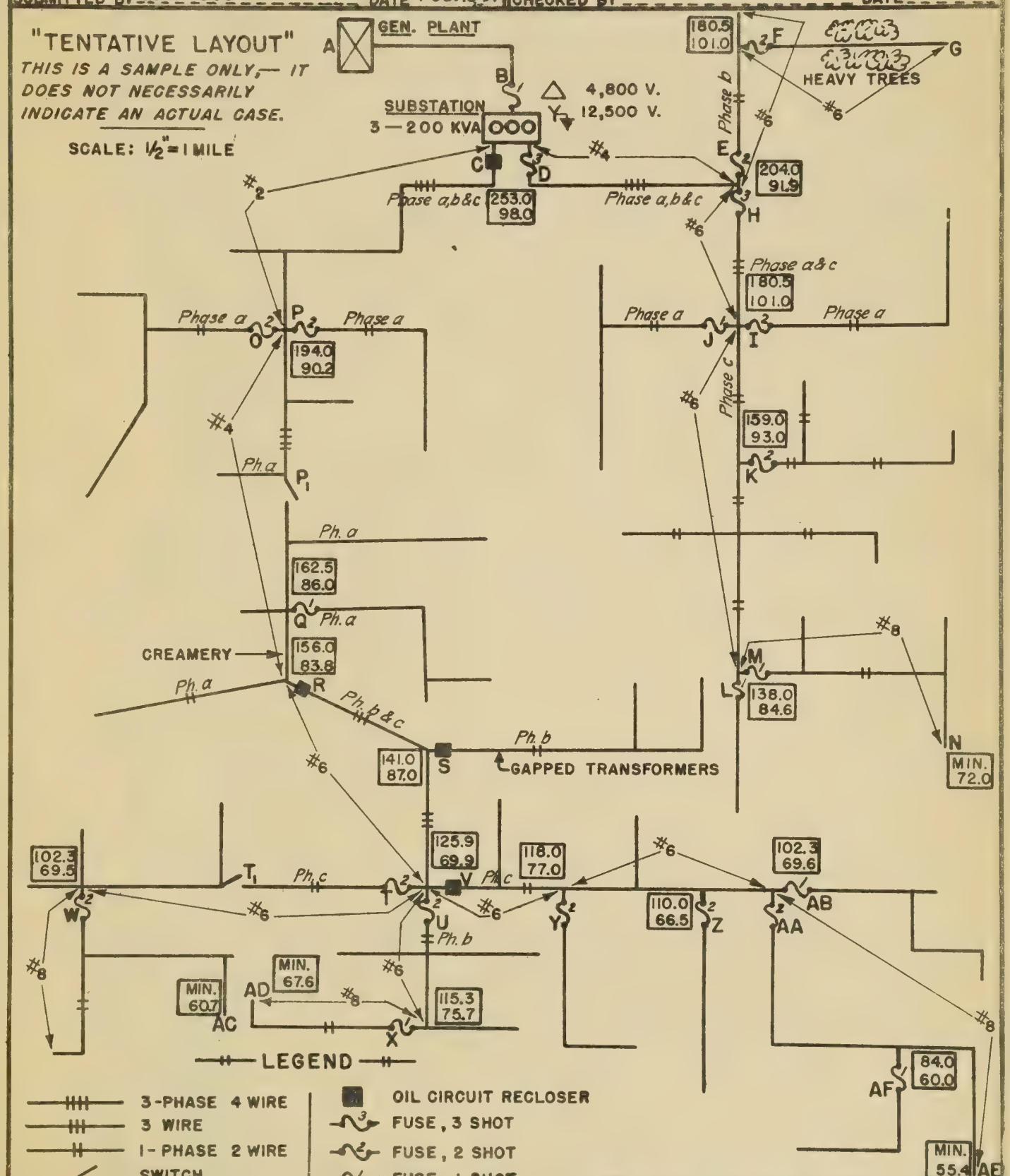

TABLE (1) **A**

COORDINATION TABLE: SUPER #XX—1D FUSE LINKS.

MAXIMUM CURRENT FOR WHICH FUSE "B" WILL PROTECT FUSE "A"

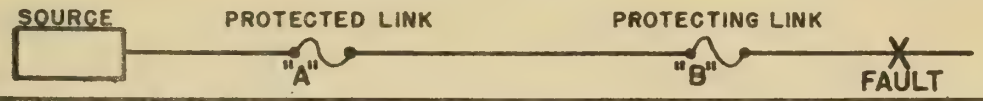

FOR EXAMPLE ONLY
DO NOT USE FOR ACTUAL CASE

RATING, AMPS OF PROTECTING FUSE LINK "B"	NO. OF SHOTS	RATING IN AMPERES OF PROTECTED FUSE LINK "A"																
		1	2	3	5	8	10	15	20	25	30	40	45	50	75	85	95	100
1	1			50	75	110	120	140	200	300	400	600	900	1300	1700	2100	2400	2800
	2			25	50	75	110	120	140	200	300	400	600	900	1300	1700	2100	2400
	3				25	50	75	110	120	140	200	300	400	600	900	1300	1700	2100
2	1				60	90	110	140	200	300	400	600	900	1300	1700	2100	2400	2800
	2				25	60	90	100	140	200	300	400	600	900	1300	1700	2100	2400
	3					25	60	90	100	140	200	300	400	600	900	1300	1700	2100
3	1					30	90	125	200	300	400	600	900	1300	1700	2100	2400	2800
	2					25	60	90	120	200	300	400	600	900	1300	1700	2100	2400
	3						25	60	90	120	200	300	400	600	900	1300	1700	2100
5	1						60	100	175	300	400	600	900	1300	1700	2100	2400	2800
	2						25	60	100	175	300	400	600	900	1300	1700	2100	2400
	3							25	60	100	175	300	400	600	900	1300	1700	2100
8	1							75	150	300	400	600	900	1300	1700	2100	2400	2800
	2							40	75	150	300	400	600	900	1300	1700	2100	2400
	3								40	75	150	300	400	600	900	1300	1700	2100
10	1								100	250	400	600	900	1300	1700	2100	2400	2800
	2								50	100	250	400	600	900	1300	1700	2100	2400
	3									50	100	250	400	600	900	1300	1700	2100
15	1									150	300	600	900	1300	1700	2100	2400	2800
	2									75	150	300	600	900	1300	1700	2100	2400
	3										75	150	300	600	900	1300	1700	2100
20	1										200	500	900	1300	1700	2100	2400	2800
	2										100	200	500	900	1300	1700	2100	2400
	3											100	200	500	900	1300	1700	2100

COORDINATION TABLE: SUPER #XX—ID FUSE LINKS.

TABLE (1) B

MAXIMUM CURRENT FOR WHICH FUSE "B" WILL PROTECT FUSE "A"

FOR EXAMPLE ONLY
DO NOT USE FOR ACTUAL CASE

RATING, AMPS OF PROTECTING FUSE LINK "B"	NO. OF SHOTS	RATING IN AMPERES OF PROTECTED FUSE LINK "A"																
		1	2	3	5	8	10	15	20	25	30	40	45	50	75	85	95	100
25	1											300	700	1300	1700	2100	2400	2800
	2											150	300	700	1300	1700	2100	2400
	3												150	300	700	1300	1700	2100
30	1												500	1000	1700	2100	2400	2800
	2												250	500	1000	1700	2100	2400
	3													250	500	1000	1700	2100
40	1													700	1400	1800	2400	2800
	2													400	700	1400	1800	2400
	3														400	700	1400	1800
45	1														1000	1400	2400	2800
	2														500	1000	1400	2400
	3															500	1000	1400
50	1															1100	2200	2800
	2															600	1100	2200
	3																600	1100
75	1																1700	2400
	2																1000	1700
	3																	1000
85	1																	2100
	2																	1000
	3																	
95 & 100		NONE																

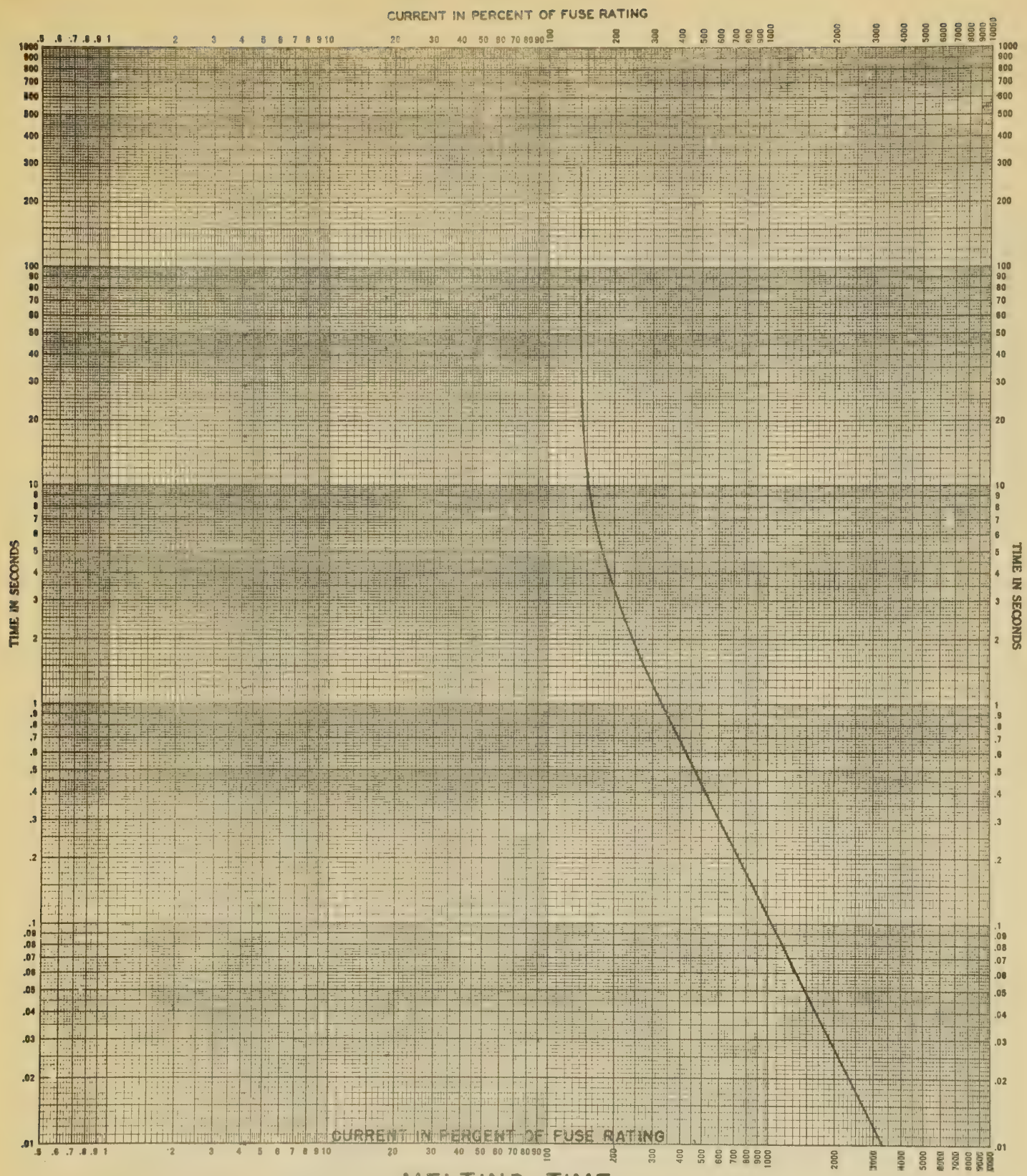

MELTING TIME
OF
PRESTO TYPE-K-POWER FUSE

FOR EXAMPLE ONLY DO NOT USE IN ACTUAL CASE.

PLATE "A"

U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM.

FEB, 1941

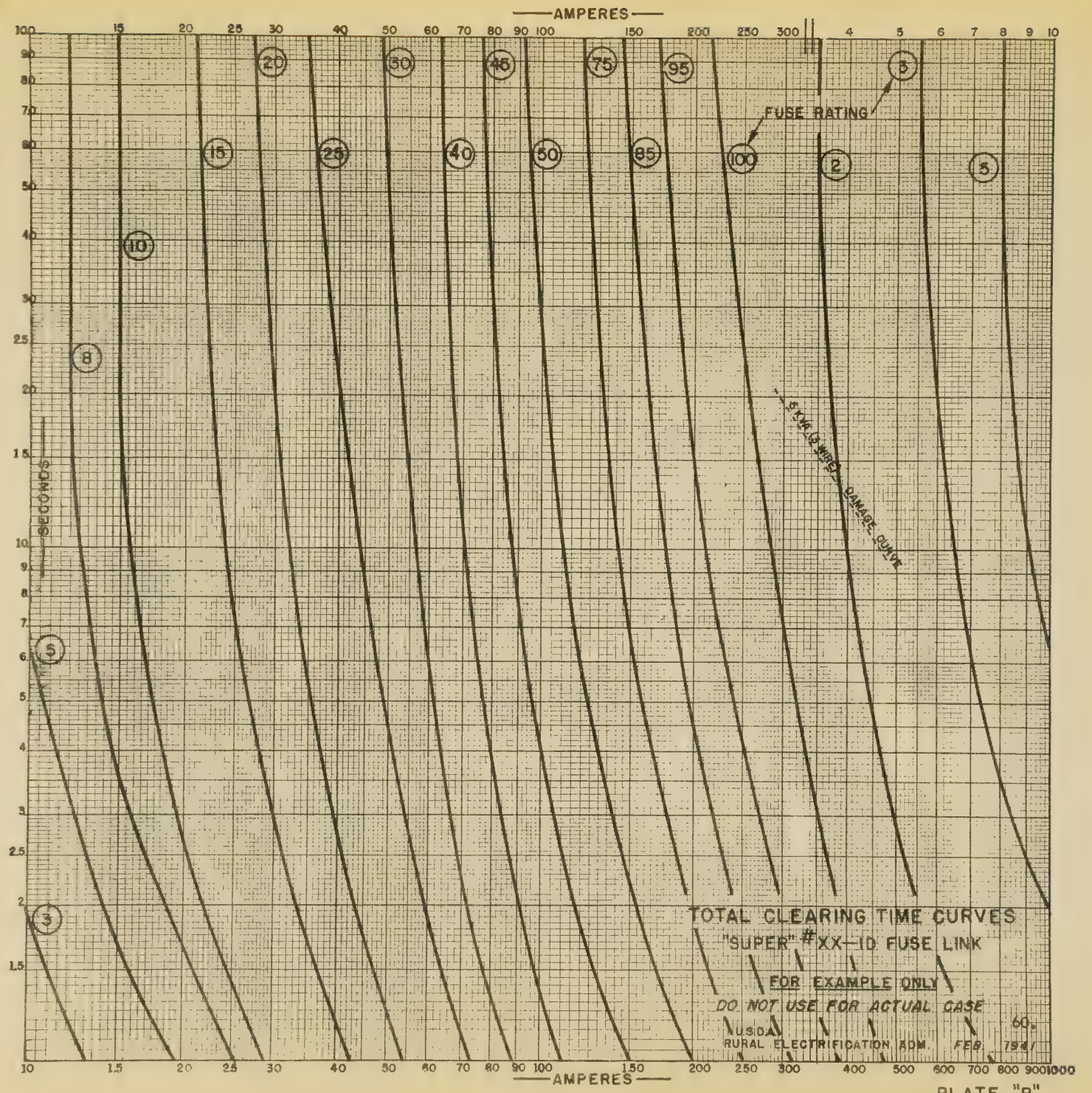
AMPERES
SECONDS
FUSE RATING
5 KA 13 WIRE DAMAGE CURVE
TOTAL CLEARING TIME CURVES
"SUPER" #XX-ID FUSE LINK
FOR EXAMPLE ONLY
DO NOT USE FOR ACTUAL CASE
U.S.D.A.
RURAL ELECTRIFICATION ADM.
FEB. 1941

PLATE "B"

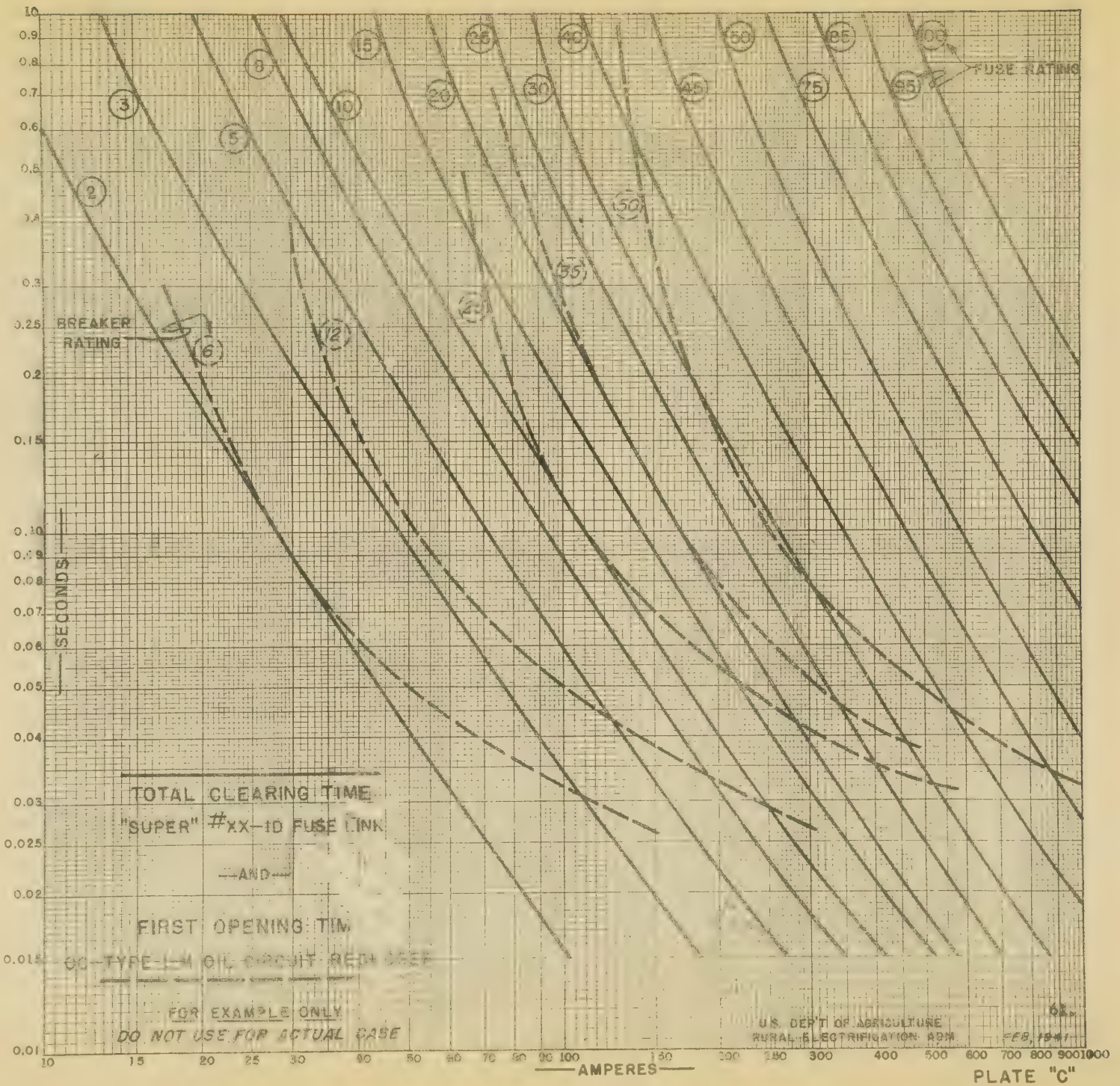
FUSE RATING
BREAKER RATING
SECONDS
AMPERES
TOTAL CLEARING TIME
"SUPER" #XX-1D FUSE LINK
—AND—
FIRST OPENING TIME
OC-TYPE-1-M OIL CIRCUIT BREAKER
FOR EXAMPLE ONLY
DO NOT USE FOR ACTUAL CASE
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM.
FEB. 1941

PLATE "C"

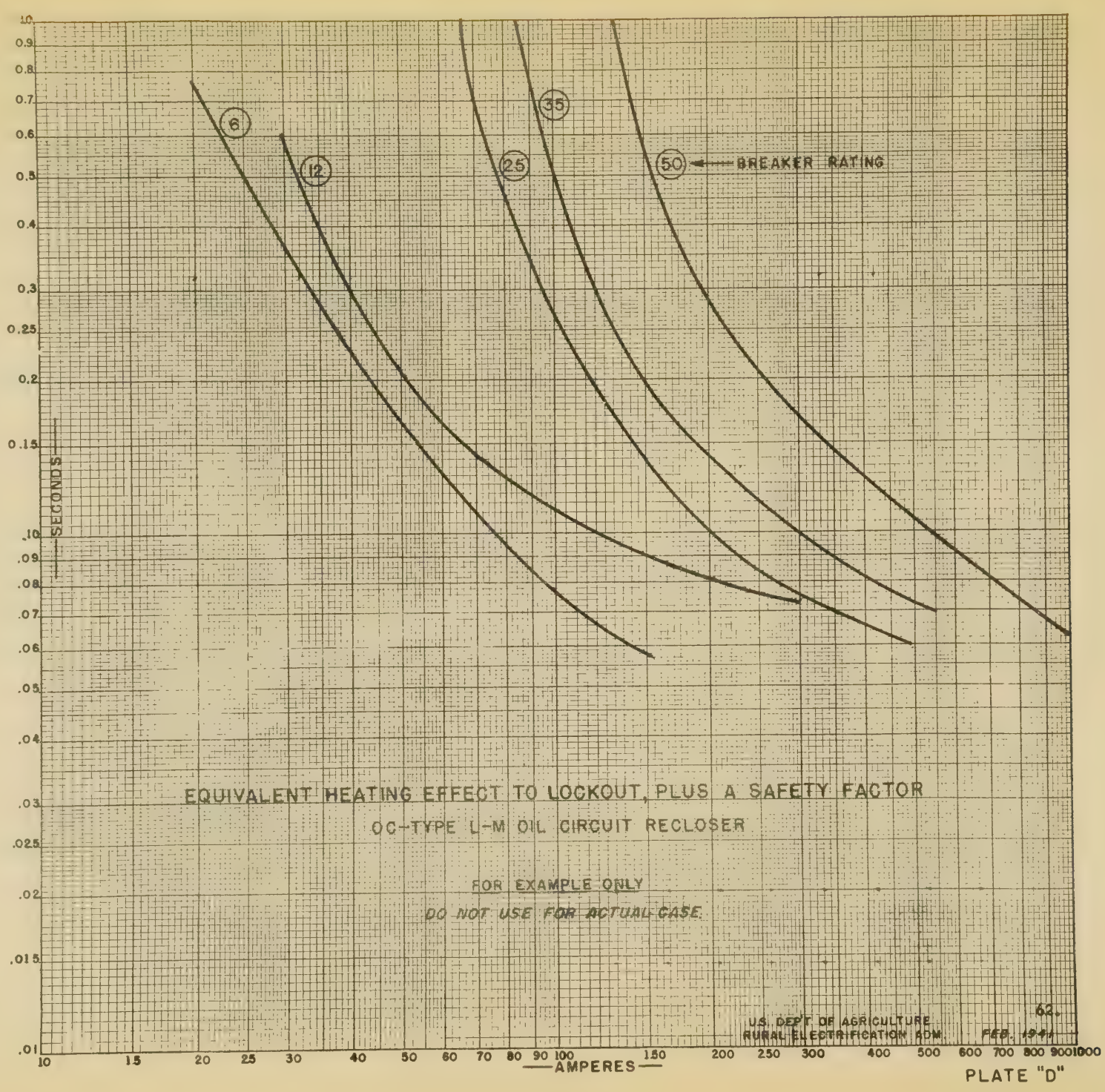
6
12
25
35
50
BREAKER RATING
SECONDS
AMPERES
EQUIVALENT HEATING EFFECT TO LOCKOUT, PLUS A SAFETY FACTOR
OC-TYPE L-M OIL CIRCUIT RECLOSER
FOR EXAMPLE ONLY
DO NOT USE FOR ACTUAL CASE
U.S. DEPT OF AGRICULTURE
RURAL ELECTRIFICATION ADM.
FEB. 1941

PLATE "D"

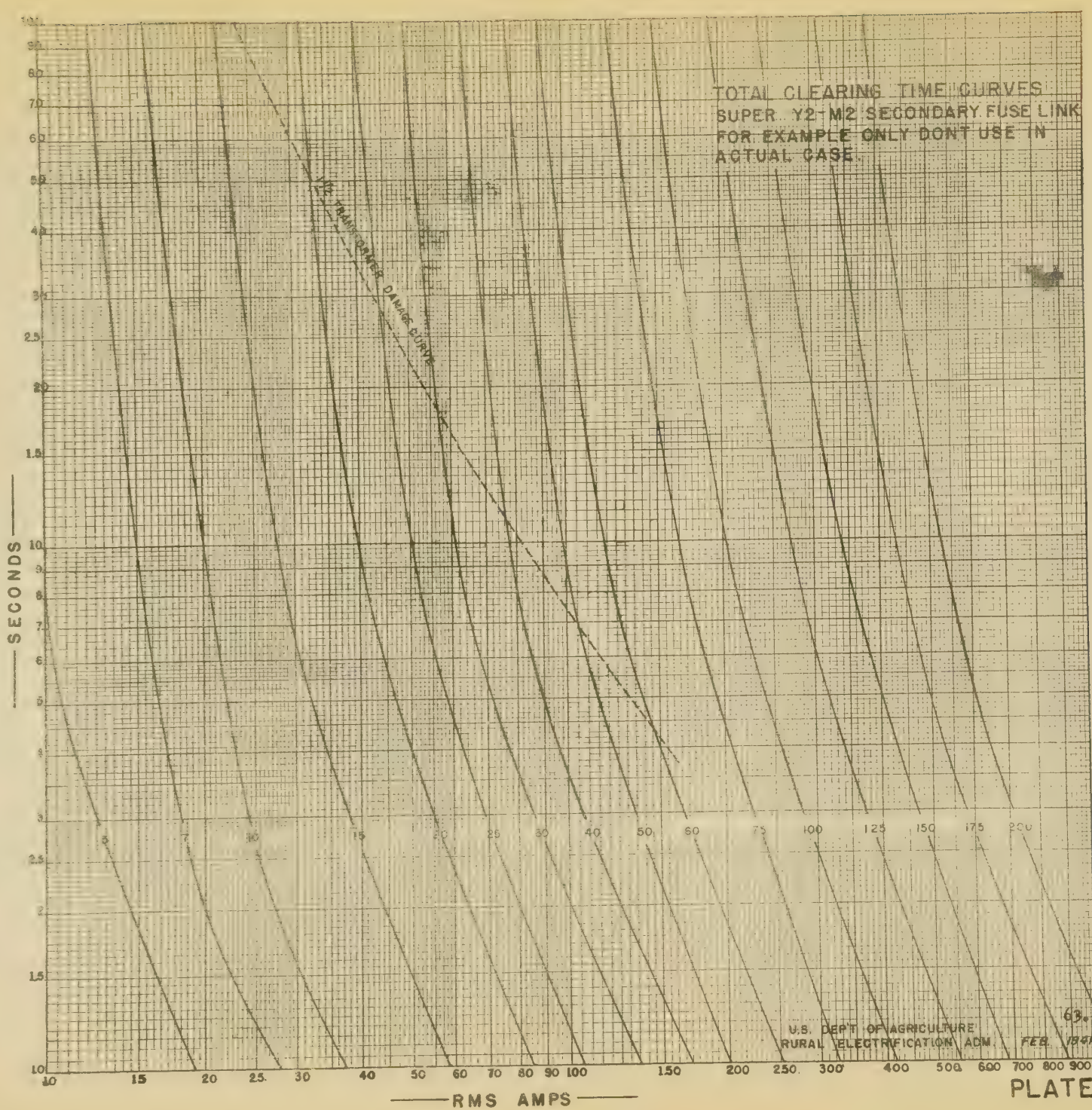
TOTAL CLEARING TIME CURVES
SUPER. Y2-M2 SECONDARY FUSE LINK
FOR EXAMPLE ONLY DONT USE IN
ACTUAL CASE.
Y2 TRANSFORMER DAMAGE CURVE
SECONDS
RMS AMPS
5
7
10
15
20
25
30
40
50
60
75
100
125
150
175
200
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM.
FEB. 1941

PLATE "E"

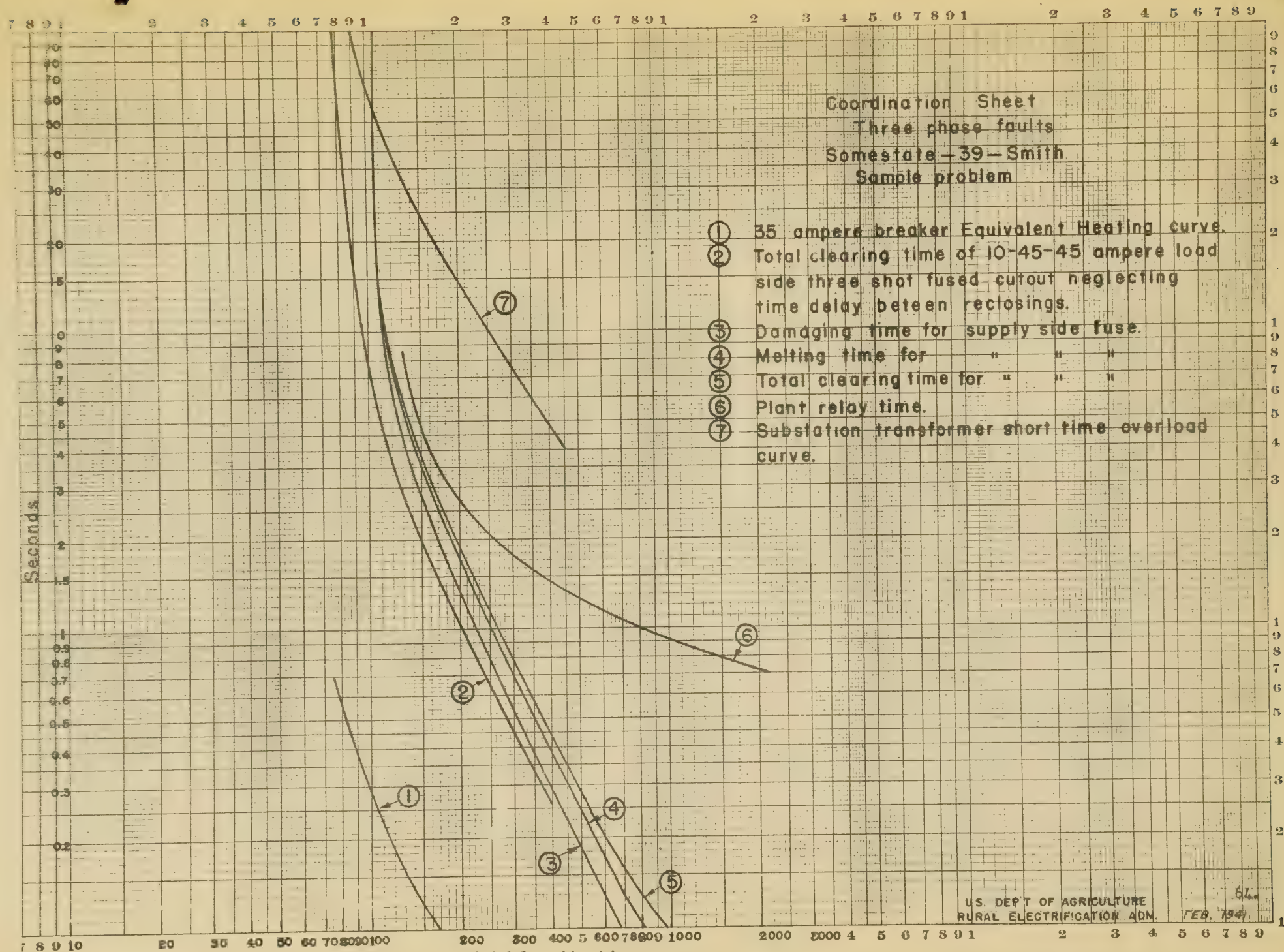
Coordination Sheet
Three phase faults
Somestate – 39 – Smith
Sample problem
① 35 ampere breaker Equivalent Heating curve.
② Total clearing time of 10-45-45 ampere load side three shot fused cutout neglecting time delay beteen reclosings.
③ Damaging time for supply side fuse.
④ Melting time for " " "
⑤ Total clearing time for " " "
⑥ Plant relay time.
⑦ Substation transformer short time overload curve.
Seconds
Amperes for Three Phase Fault on 7200 volt side
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM.
FEB. 194

PLATE F

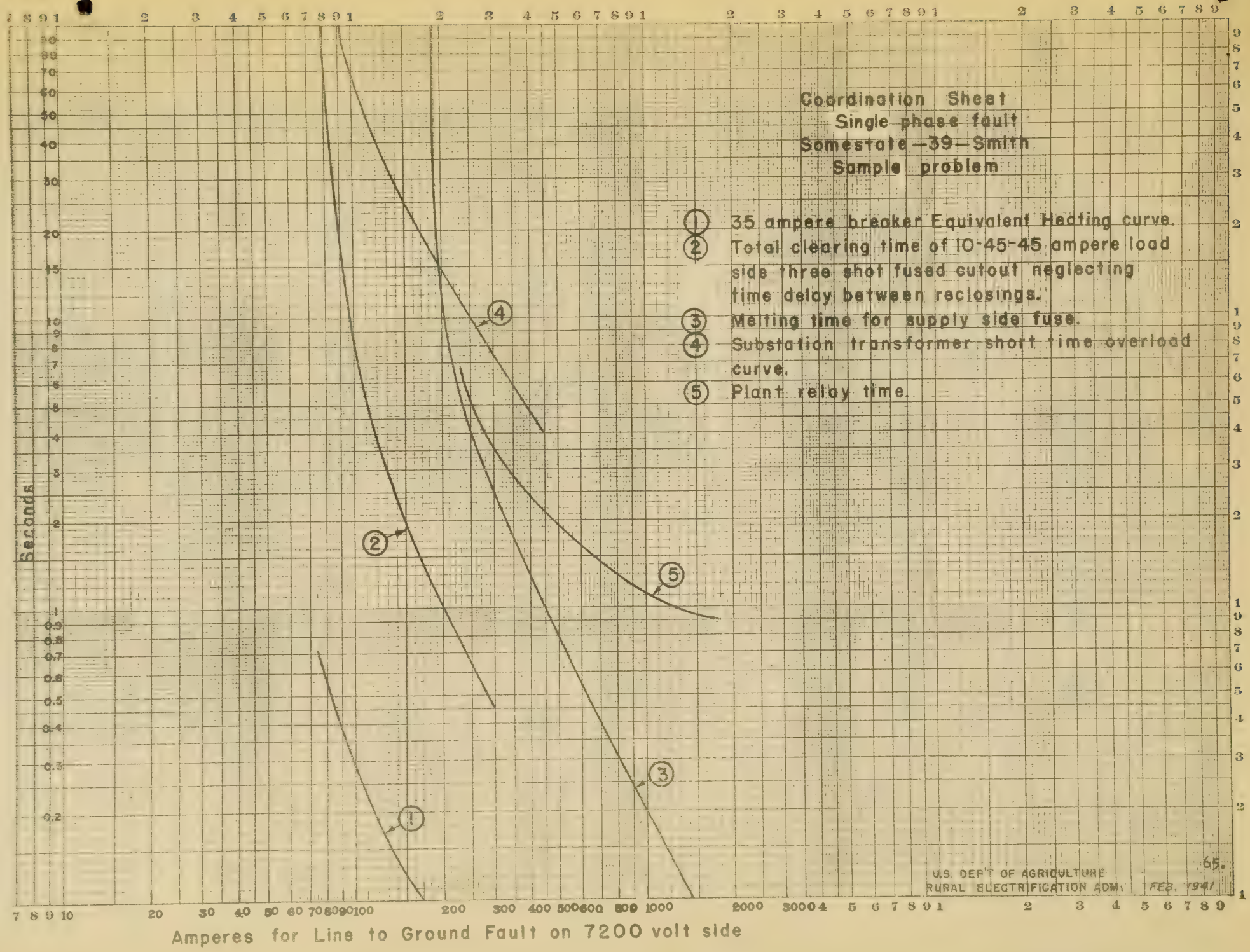
Coordination Sheet
Single phase fault
Somestate —39— Smith
Sample problem
1 35 ampere breaker Equivalent Heating curve.
2 Total clearing time of 10-45-45 ampere load side three shot fused cutout neglecting time delay between reclosings.
3 Melting time for supply side fuse.
4 Substation transformer short time overload curve.
5 Plant relay time.
Seconds
Amperes for Line to Ground Fault on 7200 volt side
U.S. DEP'T OF AGRICULTURE
RURAL ELECTRIFICATION ADM.
FEB. 1941
65.

Plate G

FORM TS-2

U.S. DEP'T OF AGRICULTURE

RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY

Sheet 1 of 6 sheets

PROJECT

SOMESTATE — 39 — SMITH

SUBMITTED BY John Doe DATE Feb. 1941

CHECKED BY DATE

TYPE OF FAULT CALCULATED
(Indicate by check(✓) in box provided below)

THREE PHASE ☐ LINE TO LINE ☐ LINE TO GROUND ☑

A — IMPEDANCE OF SOURCE

	ohms
1. PLANT	
(a) DIRECT AXIS TRANSIENT REACTANCE — FULL LOAD	16.3
(b) NEGATIVE SEQUENCE " — " "	10.1
(c) DIRECT AXIS TRANSIENT REACTANCE — MINIMUM "	48.9
(d) NEGATIVE SEQUENCE " — " "	30.3
(e) (a) + (b), EQUIVALENT REACTANCE ON LOAD SIDE	8.8
(f) (c) + (d), " " " " "	26.4
2. TIE LINE	
(g) RESISTANCE REFERRED TO LOAD VOLTAGE	3.65
(h) REACTANCE " " " "	9.14
3. TOTAL	
(i) MAXIMUM LOAD — 1. RESISTANCE EQUALS (g)	3.65
(i) MAXIMUM LOAD — 2. REACTANCE " (e) + (h)	17.93
(j) MINIMUM LOAD — 1. RESISTANCE " (g)	3.65
(j) MINIMUM LOAD — 2. REACTANCE " (f) + (h)	35.5
4. FOR LARGE SUPPLY SYSTEM ONLY	
(k) MAXIMUM LOAD REACTANCE	
(l) MINIMUM " "	

B — IMPEDANCE OF SUBSTATION

(m) Z_T	10.2
(n) R_T	2.04
(o) X_T	9.97

C — TOTAL IMPEDANCE OF SOURCE AND SUBSTATION

(p) MAXIMUM CONDITIONS	
1. $R = (n) + (i_1)$	5.69
2. $X = (o) + (i_2)$ or (k)	27.9
(q) MINIMUM CONDITIONS	
1. $R = (n) + (j_1)$	5.69
2. $X = (o) + (j_2)$ or (l)	45.47

FORM TS-2

U.S. DEP'T OF AGRICULTURE

RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY

Sheet 2 of 6 sheets

PROJECT

SOMESTATE — 39 — SMITH

SUBMITTED BY John Doe DATE Feb. 1941

CHECKED BY DATE

TYPE OF FAULT CALCULATED
(Indicate by check(✓) in box provided below)

THREE PHASE ☑ LINE TO LINE ☐ LINE TO GROUND ☐

A — IMPEDANCE OF SOURCE

	ohms
1. PLANT	
(a) DIRECT AXIS TRANSIENT REACTANCE — FULL LOAD	16.3
(b) NEGATIVE SEQUENCE " — " "	0
(c) DIRECT AXIS TRANSIENT REACTANCE — MINIMUM "	48.9
(d) NEGATIVE SEQUENCE " — " "	0
(e) (a) + (b), EQUIVALENT REACTANCE ON LOAD SIDE	16.3
(f) (c) + (d), " " " " "	48.9
2. TIE LINE	
(g) RESISTANCE REFERRED TO LOAD VOLTAGE	5.5
(h) REACTANCE " " " "	13.7
3. TOTAL	
(i) MAXIMUM LOAD — 1. RESISTANCE EQUALS (g)	5.5
(i) MAXIMUM LOAD — 2. REACTANCE " (e) + (h)	30.0
(j) MINIMUM LOAD — 1. RESISTANCE " (g)	5.5
(j) MINIMUM LOAD — 2. REACTANCE " (f) + (h)	62.6
4. FOR LARGE SUPPLY SYSTEM ONLY	
(k) MAXIMUM LOAD REACTANCE	
(l) MINIMUM " "	

B — IMPEDANCE OF SUBSTATION

(m) Z_T	10.2
(n) R_T	2.04
(o) X_T	9.97

C — TOTAL IMPEDANCE OF SOURCE AND SUBSTATION

(p) MAXIMUM CONDITIONS	
1. $R = (n) + (i_1)$	7.5
2. $X = (o) + (i_2)$ or (k)	40.0
(q) MINIMUM CONDITIONS	
1. $R = (n) + (j_1)$	7.5
2. $X = (o) + (j_2)$ or (l)	72.6

FORM TS-2

U.S. DEP'T OF AGRICULTURE

RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY

Sheet 3 of 6 sheets

PROJECT

SOMESTATE — 39 — SMITH

SUBMITTED BY John Doe DATE Feb. 1941

CHECKED BY _____ DATE _____

TYPE OF FAULT CALCULATED
(Indicate by check(✓) in box provided below)

THREE PHASE ☐ LINE TO LINE ☑ LINE TO GROUND ☐

A — IMPEDANCE OF SOURCE

	ohms
1. PLANT	
(a) DIRECT AXIS TRANSIENT REACTANCE — FULL LOAD	16.3
(b) NEGATIVE SEQUENCE " — " "	10.1
(c) DIRECT AXIS TRANSIENT REACTANCE — MINIMUM "	48.9
(d) NEGATIVE SEQUENCE " — " "	30.3
(e) (a) + (b), EQUIVALENT REACTANCE ON LOAD SIDE	15.2
(f) (c) + (d), " " " " "	45.7
2. TIE LINE	
(g) RESISTANCE REFERRED TO LOAD VOLTAGE	6.3
(h) REACTANCE " " " "	15.8
3. TOTAL	
(i) MAXIMUM LOAD — 1. RESISTANCE EQUALS (g)	6.3
(i) MAXIMUM LOAD — 2. REACTANCE " (e) + (h)	31.0
(j) MINIMUM LOAD — 1. RESISTANCE " (g)	6.3
(j) MINIMUM LOAD — 2. REACTANCE " (f) + (h)	61.5
4. FOR LARGE SUPPLY SYSTEM ONLY	
(k) MAXIMUM LOAD REACTANCE	
(l) MINIMUM " "	

B — IMPEDANCE OF SUBSTATION

(m) Z_T	11.8
(n) R_T	2.4
(o) X_T	11.5

C — TOTAL IMPEDANCE OF SOURCE AND SUBSTATION

(p) MAXIMUM CONDITIONS	
1. $R = (n) + (i_1)$	8.7
2. $X = (o) + (i_2)$ or (k)	42.5
(q) MINIMUM CONDITIONS	
1. $R = (n) + (j_1)$	8.7
2. $X = (o) + (j_2)$ or (l)	73.0

FORM TS-3

U.S. DEPARTMENT OF AGRICULTURE
RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY

SHEET 4 OF 6 SHEETS

PROJECT
Somestate-39-Smith

SUBMITTED BY John Doe DATE Feb. 1941 CHECKED BY _____ DATE _____

r	s	t	u	v	w	x	y	z	aa	ab	ac	ad	ae	af	ag	ah
POINT	PRECEDING POINT ON LINE TOWARD SUBSTATION	MILES FROM PREVIOUS POINT ON LINE TOWARD SUBSTATION	COPPER CONDUCTIVITY SIZE, SECTION FROM PREVIOUS POINT	TYPE OF FAULT CALCULATED	RESISTANCE "R", SECTION FROM PREVIOUS POINT	RESISTANCE "R", BACK TO SUBSTATION	FOR MAX. CONDITION, TOTAL RESISTANCE TO SOURCE = x + p_1	FOR MIN. CONDITION, TOTAL RESIST. TO SOURCE = y + FAULT RESIST.	REACTANCE "X", SECTION FROM PREVIOUS POINT	REACTANCE "X", BACK TO SUBSTATION	FOR MAX. CONDITION, TOTAL REACTANCE TO SOURCE = ab + p_2	FOR MIN. CONDITION, TOTAL REACTANCE TO SOURCE = ab + q_2	FOR MAX. CONDITION, TOTAL IMPEDANCE TO SOURCE = $\sqrt{y^2+ac^2}$	FOR MIN. CONDITION, TOTAL IMPEDANCE TO SOURCE = $\sqrt{z^2+ad^2}$	MAX. CURRENT "I" = $\frac{\text{VOLTAGE}}{ae}$	MIN. CURRENT "I" = $\frac{\text{VOLTAGE}}{af}$
SUB							5.7	35.7			27.9	45.5	28.5	57.8	253.0	124.5
D															"	"
O	SUB	6	#2		6.00	6.0	11.7	41.7	7.32	7.3	35.2	52.8	37.1	67.3	194.0	107.0
P	"														"	"
Q	O	4	#4		6.52	12.5	18.2	48.2	5.24	12.5	40.4	58.0	44.3	75.4	162.5	95.5
R	Q	1	#4		1.63	14.1	19.8	49.8	1.31	13.8	41.7	59.3	46.1	77.4	156.0	93.0
S															141.0*	87.0*
T	R	4.5	#6	Line—to—Ground	11.00	25.1	30.8	60.8	6.57	20.4	48.3	65.9	57.3	89.6	125.9	80.4
U	R														"	"
V	R														"	"
W	T	5	#6		12.25	37.4	43.1	73.1	7.30	27.7	55.6	73.2	70.4	103.5	102.3	69.5
AC	W	4	#8		14.96	52.4	58.1	88.1	6.20	33.9	61.8	79.4	84.9	118.6	84.9	60.7
X	U	2	#6		4.90	30.0	35.7	65.7	2.92	23.3	51.2	68.8	62.4	95.1	115.3	75.7
AD	X	3	#8		11.22	41.2	46.9	76.9	4.65	28.0	55.9	73.5	73.0	106.4	98.6	67.6
Y			#6												118.0*	77.0*

*ESTIMATED

FORM TS-3

U.S. DEPARTMENT OF AGRICULTURE
RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY

SHEET 5 OF 6 SHEETS

PROJECT: Somestate-39-Smith

SUBMITTED BY John Doe, DATE Feb. 1941 | CHECKED BY _____, DATE _____

r	s	t	u	v	w	x	y	z	aa	ab	ac	ad	ae	af	ag	ah
POINT	PRECEDING POINT ON LINE TOWARD SUBSTATION	MILES FROM PREVIOUS POINT ON LINE TOWARD SUBSTATION	COPPER CONDUCTIVITY SIZE, SECTION FROM PREVIOUS POINT	TYPE OF FAULT CALCULATED	RESISTANCE "R", SECTION FROM PREVIOUS POINT	RESISTANCE "R", BACK TO SUBSTATION	FOR MAX. CONDITION, TOTAL RESISTANCE TO SOURCE = x + p_1	FOR MIN. CONDITION, TOTAL RESIST TO SOURCE = y + FAULT RESIST.	REACTANCE "X", SECTION FROM PREVIOUS POINT	REACTANCE "X", BACK TO SUBSTATION	FOR MAX. CONDITION, TOTAL REACTANCE TO SOURCE = ab + p_2	FOR MIN. CONDITION, TOTAL REACTANCE TO SOURCE = ab + q_2	FOR MAX. CONDITION, TOTAL IMPEDANCE TO SOURCE = $\sqrt{y^2+ac^2}$	FOR MIN. CONDITION, TOTAL IMPEDANCE TO SOURCE = $\sqrt{z^2+ad^2}$	MAX. CURRENT "I" = $\frac{\text{VOLTAGE}}{ae}$	MIN. CURRENT "I" = $\frac{\text{VOLTAGE}}{af}$
Z															110.0*	66.5*
AA	V	5	#6		12.25	37.4	43.1	73.1	7.30	27.7	55.6	73.2	70.4	103.5	102.3	69.6
AB	V														"	"
AF															84.0*	60.0*
AE	AA	7	#8		26.18	63.6	69.3	99.3	10.85	38.6	66.5	84.1	96.0	130.0	75.0	55.4
E	D	4	#4	Line—to—Ground	6.52	6.5	12.2	42.2	5.24	5.2	33.1	50.7	35.3	66.0	204.0	109.0
H	D														"	"
F	E	2	#6		4.90	11.4	17.1	47.1	2.92	8.1	36.0	53.6	39.9	71.3	180.5	101.0
J	H	2	#6		4.90	11.4	17.1	47.1	2.92	8.1	36.0	53.6	39.9	71.3	180.5	101.0
I	H														"	"
K															159.0*	93.0*
L	J	5	#6		12.25	23.7	29.4	59.4	7.30	15.4	43.3	60.9	52.3	85.1	138.0	84.6
M	J														"	"
N	M	4	#8		14.96	38.7	44.4	74.4	6.20	21.6	49.5	67.1	66.6	100.0	108.0	72.0

*ESTIMATED

FORM TS-3

U.S. DEPARTMENT OF AGRICULTURE
RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY

SHEET 6 OF 6 SHEETS

PROJECT: Somestate-39-Smith

SUBMITTED BY John Doe, DATE Feb. 1941

CHECKED BY _____, DATE _____

r	s	t	u	v	w	x	y	z	aa	ab	ac	ad	ae	af	ag	ah
POINT	PRECEDING POINT ON LINE TOWARD SUBSTATION	MILES FROM PREVIOUS POINT ON LINE TOWARD SUBSTATION	COPPER CONDUCTIVITY SIZE, SECTION FROM PREVIOUS POINT	TYPE OF FAULT CALCULATED	RESISTANCE "R", SECTION FROM PREVIOUS POINT	RESISTANCE "R", BACK TO SUBSTATION	FOR MAX. CONDITION, TOTAL RESISTANCE TO SOURCE = X + P_1	FOR MIN. CONDITION, TOTAL RESIST. TO SOURCE = Y + FAULT RESIST.	REACTANCE "X", SECTION FROM PREVIOUS POINT	REACTANCE "X", BACK TO SUBSTATION	FOR MAX. CONDITION, TOTAL REACTANCE TO SOURCE = ab + p_2	FOR MIN. CONDITION, TOTAL REACTANCE TO SOURCE = ab + q_2	FOR MAX. CONDITION, TOTAL IMPEDANCE TO SOURCE = $\sqrt{y^2+ac^2}$	FOR MIN. CONDITION, TOTAL IMPEDANCE TO SOURCE = $\sqrt{z^2+ad^2}$	MAX. CURRENT "I" = $\frac{\text{VOLTAGE}}{ae}$	MIN. CURRENT "I" = $\frac{\text{VOLTAGE}}{af}$
SUB				3-Phase			7.5	7.5			40.0	72.6	40.7	73.0	177.0	98.7
O	SUB	6	#2		5.2	5.2	12.7	12.7	4.6	4.6	46.6	77.2	48.3	78.4	149.0	91.9
R	O	5	#4		6.8	12.0	19.5	19.5	4.0	8.6	50.6	81.2	54.2	83.4	133.0	86.4
H	SUB	4	#4		5.4	5.4	12.9	12.9	3.2	3.2	43.2	75.8	45.1	77.0	160.0	93.5
SUB				Line-to-Line			8.7	8.7			42.5	73.0	43.3	73.5	166.0	98.0
O	SUB	6	#2		6.0	6.0	14.7	14.7	5.3	5.3	47.8	78.3	50.0	79.7	144.0	90.2
R	O	5	#4		7.9	13.9	22.6	22.6	4.6	9.9	52.4	82.9	57.0	86.0	126.0	83.8
T	R	4.5	#6		11.3	25.2	33.9	33.9	4.3	14.2	56.7	97.1	66.1	103.0	109.0	69.9
H	SUB	4	#4		6.2	6.2	14.9	14.9	3.7	3.7	46.2	76.7	48.5	78.3	148.0	91.9
I	H	2	#6		5.0	11.2	19.9	19.9	1.9	5.6	51.8	78.6	55.5	81.0	130.0	88.8

FORM TS-4

U.S. DEP'T OF AGRICULTURE

RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY

Sheet 1 of 1 sheets

PROJECT

SOMESTATE—39—SMITH

SUBMITTED BY John Doe DATE Feb. 1941

CHECKED BY DATE

This Study is based on the use of the following makes of Sectionalizing Equipment:—

	BREAKERS	FUSE LINKS
1. Substation—Supply Side		PRESTO—TYPE "K"
2. Substation—Load Side	OC—TYPE LM.	SUPER XX—10
3. Lines	" " "	" "

POINT	PRESENT DEVICE		DEVICE TO BE INSTALLED		REMARKS
	TYPE	DISPOSITION	TYPE	RATING	
B			1—SHOT	200 A.	
C			BREAKER	35 A.	
D			3—SHOT	10—45—45 A.	
E			2—SHOT	30 A.	
F			2—SHOT	10 A.	
H			2—SHOT	30 A.	
I	NONE		2—SHOT	10 A.	
J			2—SHOT	10 A.	
K			2—SHOT	10 A.	
L			2—SHOT	10 A.	
M			2—SHOT	10 A.	
O			2—SHOT	20 A.	
P			2—SHOT	20 A.	
P-1			DISCONNECT		
Q			1—SHOT	20 A.	
R			BREAKER	25 A.	
S			"	12 A.	
T			2—SHOT	10 A.	
T-1			DISCONNECT		
U			2—SHOT	10 A.	
V			BREAKER	12 A.	
W			2—SHOT	2 A.	
X	NONE		DISCONNECT		
Y			2—SHOT	3 A.	
Z			2—SHOT	3 A.	
AA			2—SHOT	3 A.	
AB			2—SHOT	3 A.	
AF			DISCONNECT		

DEPARTMENT OF AGRICULTURE

RURAL ELECTRIFICATION ADMINISTRATION

SECTIONALIZING STUDY "KEY MAP" B

PROJECT

SOMESTATE-39-SMITH

SUBMITTED BY John Doe, DATE Feb. 1941 CHECKED BY _____, DATE _____